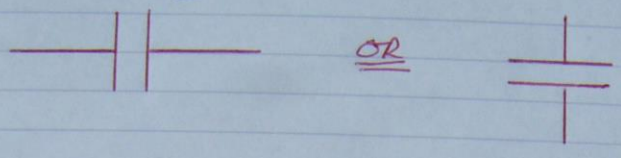




# Capacitors - B McMULLEN

①

## Circuit symbol




A capacitor stores electrical charge and electrical energy.
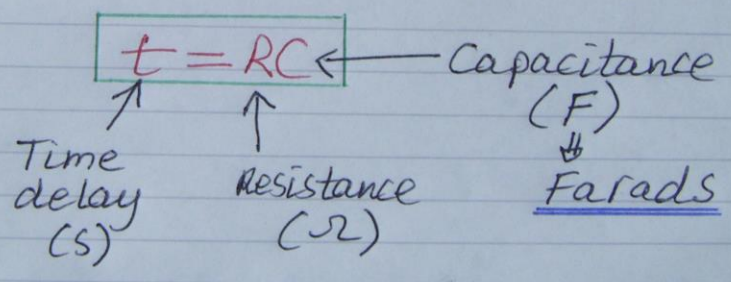
## Think Abstract !!

- \* Capacitor  $\Rightarrow$  Bucket
- Charge stored in capacitor  $\Rightarrow$  Water in bucket
- Resistance  $\Rightarrow$  hole in the bucket

Capacitors are used in time-delay circuits.



- For a capacitor to charge up quickly  
ie a small time-delay  
 $\Rightarrow t \downarrow \therefore R$  and/or  $C \downarrow$
- For a capacitor to charge up slowly  
ie a large time-delay  
 $\Rightarrow t \uparrow \therefore R$  and/or  $C \uparrow$

## Applying to the Bucket theory (2)


- To fill a small bucket with a small hole  $\Rightarrow$  small time  
ie small capacitance with a small resistance  $\Rightarrow$  small time-delay.
- To fill a large bucket with a large hole  $\Rightarrow$  large time  
ie large capacitance with a large resistance  $\Rightarrow$  large time-delay.

## Frequency and time-delay


$$f = \frac{1}{T} \Rightarrow f \propto \frac{1}{T}$$
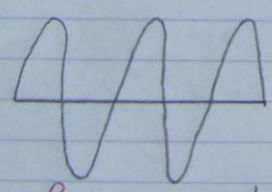
## Conclusion

Time-delay  $\downarrow$   $\therefore$  frequency  $\uparrow$   
and  
Time-delay  $\uparrow$   $\therefore$  frequency  $\downarrow$




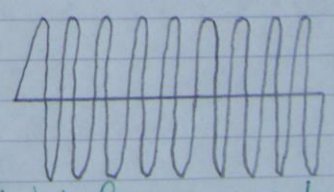
Low frequency  $\rightarrow$  high period



high frequency  $\rightarrow$  low period.

## Capacitance Equation

(3)

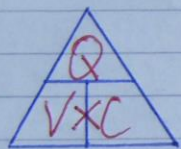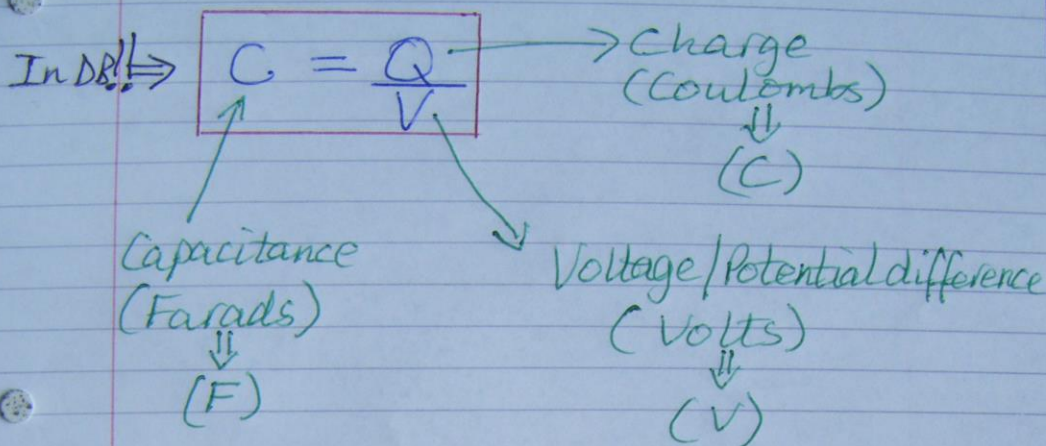

QVC  
 $\downarrow$

Shopping channel!!

1/  $Q = VC$     2/  $C = Q/V$     3/  $V = Q/C$

## Alternative units for Capacitance

From  $C = \frac{Q}{V} \Rightarrow 1F = \frac{1C}{1V}$

$\Rightarrow \text{xx} 1F = 1CV^{-1} \text{xx}$

$\Rightarrow 1 \text{ Farad} = 1 \text{ Coulomb per Volt.}$

## magnitude of Capacitance

(4)

DO NOT use the words size or value when you talk about capacitance or Resistance.

ie Increase or decrease the Capacitance or Resistance.

- pF = picofarads =  $\times 10^{-12} \text{ F}$   $\Rightarrow$  Low Capacitance
- nF = nanofarads =  $\times 10^{-9} \text{ F}$
- $\mu\text{F}$  = microfarads =  $\times 10^{-6} \text{ F}$
- mF = millifarads =  $\times 10^{-3} \text{ F}$   $\Rightarrow$  high Capacitance.

\* I have only ever seen one capacitor which has a capacitance of greater than one Farad. \*

### Ex1

Q Calculate the charge stored in a  $400 \mu\text{F}$  capacitor when a voltage of 7V is dropped across it.

A

$$Q = ?$$


$$V = 7\text{V}$$

$$C = 400 \mu\text{F} = 400 \times 10^{-6} \text{ F}$$

$$Q = VC$$

$$\Rightarrow Q = 7 \times 400 \times 10^{-6}$$
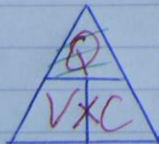
$$\Rightarrow \underline{\underline{Q = 2.8 \times 10^{-3} \text{ C}}}$$



(5)

Ex2

Q A capacitor is marked 2500nF on its side. How long will it take for an average current of 12A to charge it up to 150V

A  $C = 2500\text{nF}$   
 $I = 12\text{A}$

$V = 150\text{V}$

$t = ?$

$Q = ?$

STEP 1  $\Rightarrow C = \frac{Q}{V}$


$\Rightarrow Q = VC = 150 \times 2500 \times 10^{-9}$

$\Rightarrow Q = 3.75 \times 10^{-4}\text{C}$

STEP 2  $\Rightarrow Q = It$

$\Rightarrow t = \frac{Q}{I} = \frac{3.75 \times 10^{-4}}{12} = 3.125 \times 10^{-5}$

Energy stored in a capacitor

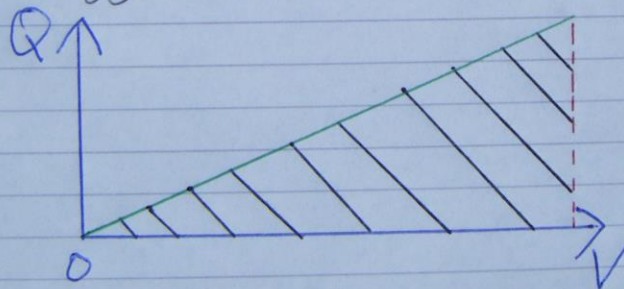

Energy stored in a capacitor =  
Area under a Q-V graph

$E_{CAP} = \frac{1}{2} QV$

6

• From  $C = \frac{Q}{V} \Rightarrow Q = VC$

Sub  $Q = VC$  into  $E_{CAP} = \frac{1}{2} QV$

$$\Rightarrow E_{CAP} = \frac{1}{2} (VC)V \Rightarrow \boxed{E_{CAP} = \frac{1}{2} CV^2}$$

• From  $C = \frac{Q}{V} \Rightarrow V = \frac{Q}{C}$

Sub  $V = \frac{Q}{C}$  into  $E_{CAP} = \frac{1}{2} QV$

$$\Rightarrow E_{CAP} = \frac{1}{2} Q \left( \frac{Q}{C} \right) \Rightarrow \boxed{E_{CAP} = \frac{1}{2} \frac{Q^2}{C}}$$

### Summary

\* •  $E_{CAP} = \frac{1}{2} QV \rightarrow$  most

\* •  $E_{CAP} = \frac{1}{2} CV^2 \rightarrow$  common  
in use !!

•  $E_{CAP} = \frac{1}{2} \cdot \frac{Q^2}{C}$

Ex3

Q Calculate the energy stored in a 650µF capacitor when fully charged by a 8V dc supply.

A  $E_{CAP} = ?$   $E_{CAP} = \frac{1}{2} CV^2$   
 $C = 650\mu F = 650 \times 10^{-6} F$   $\Rightarrow E_{CAP} = \frac{1}{2} \times 650 \times 10^{-6} \times 8^2$   
 $V = 8V$   $\Rightarrow \underline{E_{CAP} = 2.08 \times 10^{-2} J}$

Ex4

Q A 2500µF capacitor has  $7.2 \times 10^{-5} J$  of electrical energy stored in it. Calculate the charge stored in the capacitor.

A  $E_{CAP} = 7.2 \times 10^{-5} J$   
 $C = 2500\mu F = 2500 \times 10^{-6} F$   
 $Q = ?$

METHOD 1

$E_{CAP} = \frac{1}{2} \cdot \frac{Q^2}{C} \Rightarrow 7.2 \times 10^{-5} = \frac{1}{2} \cdot \frac{Q^2}{2500 \times 10^{-6}}$

$\Rightarrow$  multiply each side by 2 to get rid of the  $\frac{1}{2}$ .

$\Rightarrow 2 \times 7.2 \times 10^{-5} = 2 \times \frac{1}{2} \cdot \frac{Q^2}{2500 \times 10^{-6}}$

(8)

$$\Rightarrow 14.4 \times 10^{-5} = \frac{Q^2}{2500 \times 10^{-6}}$$

$$\Rightarrow Q^2 = 14.4 \times 10^{-5} \times 2500 \times 10^{-6} = 3.6 \times 10^{-7}$$

$$\Rightarrow Q = \sqrt{3.6 \times 10^{-7}} = \underline{\underline{6 \times 10^{-4} \text{C}}}$$

### METHOD 2

STEP 1

$$E_{\text{CAP}} = \frac{1}{2} CV^2 \quad \text{To find } V$$

$$\Rightarrow 7.2 \times 10^{-5} = \frac{1}{2} \times 2500 \times 10^{-6} \times V^2$$

MULTIPLY EACH  
SIDE BY 2

$$\Rightarrow 14.4 \times 10^{-5} = 2500 \times 10^{-6} \times V^2$$

$$\Rightarrow V^2 = \frac{14.4 \times 10^{-5}}{2500 \times 10^{-6}} = 0.0576 \Rightarrow \underline{\underline{V = 0.24 \text{V}}}$$

STEP 2

$$E_{\text{CAP}} = \frac{1}{2} QV \quad \text{To find } Q$$

$$\Rightarrow 7.2 \times 10^{-5} = \frac{1}{2} \times Q \times 0.24$$

MULTIPLY EACH  
SIDE BY 2

$$\Rightarrow 14.4 \times 10^{-5} = Q \times 0.24$$

$$\Rightarrow Q = \frac{14.4 \times 10^{-5}}{0.24}$$


$$\Rightarrow \underline{\underline{Q = 6 \times 10^{-4} \text{C}}}$$

\* I would advise that you should use METHOD 1 to do the calculation in one stage. \*



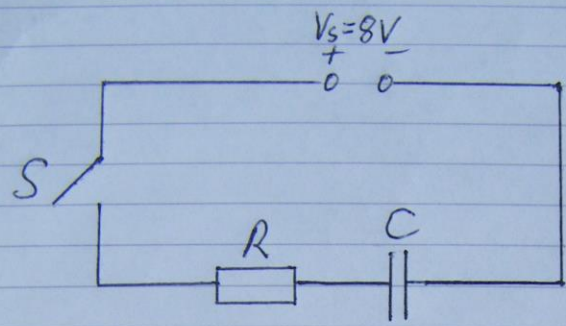(9)

Ex 5 (NB!! Explains the difference between  $E_W = QV$  and  $E_{CAP} = \frac{1}{2}QV$ )



Q When the switch is closed the capacitor charges up constantly at  $6 \times 10^{-4} C$ .


- a) Calculate the electrical work done required to fully charge up the capacitor from being uncharged.
- b) Calculate the energy stored in the capacitor when it is fully charged.
- c) Explain the difference in the answers found in a) and b).

Ans a)  $E_W = QV = 6 \times 10^{-4} \times 8 = \underline{4.8 \times 10^{-3} J}$

b)  $E_{CAP} = \frac{1}{2}QV = \frac{1}{2} \times 6 \times 10^{-4} \times 8 = \underline{2.4 \times 10^{-3} J}$

c) Half of the electrical work done is stored as electrical energy in the capacitor with the other half given off as heat energy through the resistor.
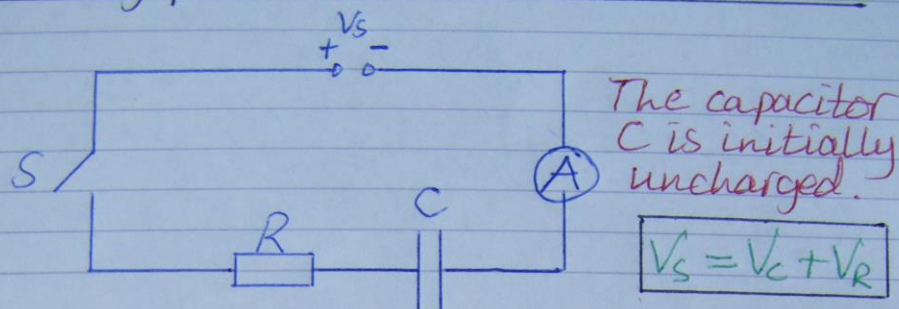
## Voltage/Potential Dividers with R and C (10)



1) At the instant when S is closed, a current will flow.

$$I = \frac{V_r}{R} \quad \text{As } C \text{ is uncharged then } V_c = 0 \Rightarrow V_r = V_s$$

As  $V_r$  is at a maximum at this point then the current is at a maximum

$$\text{ie } I = \frac{V_r}{R} \leftarrow \text{max} \quad \therefore I \propto V_r$$

$R \leftarrow \text{constant}$

2) As the capacitor charges up  $V_c$  increases from 0V and  $V_r$  decreases from its original  $V_s$ .

$$\leftarrow = \uparrow + \downarrow$$
$$V_s = V_c + V_r \quad (\text{charging!!})$$

As  $I = \frac{V_r}{R}$  as  $V_r$  decreases then the current  $I$  decreases.

$$\text{ie } I \propto V_r$$


3) When the capacitor fully charges up,  $V_c$  is at a maximum.

$\leftrightarrow = \uparrow + \downarrow$   
 $V_s = V_c + V_R$


ie ( $V_c = V_s$ )

As  $V_R = 0$  then  $I = \frac{V_R}{R} \Rightarrow I = 0$ .

Graphically

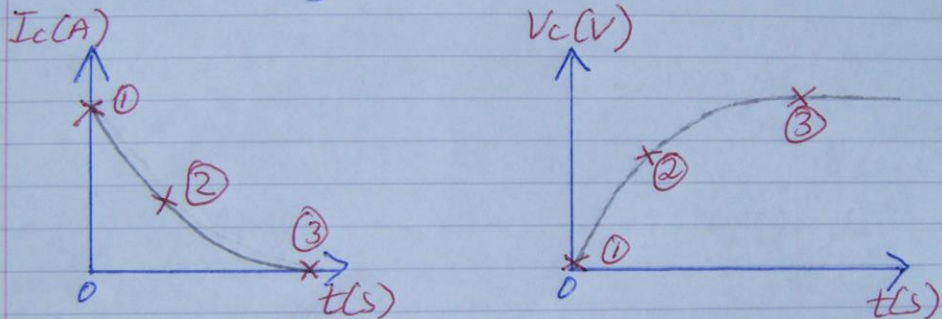

Varying R and C in charging graphs.

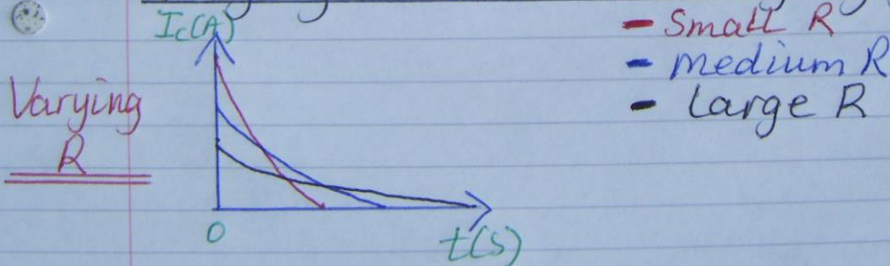

• Small R  $\Rightarrow I_{max}$  increases ( $I = \frac{V_R}{R}$ )

Also from  $t = RC$  ( $t \propto R$ ).

$\Rightarrow$  As R is small then the time delay is small.


• Large R  $\Rightarrow I_{max}$  decreases ( $I = \frac{V_R}{R}$ )

Also from  $t = RC$  ( $t \propto R$ )

$\Rightarrow$  As R is large then the time delay is large.

Varying C

$I_C(A)$

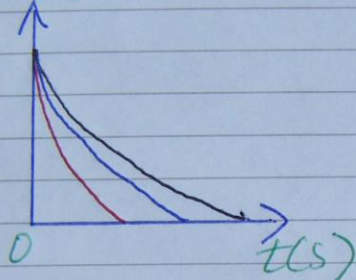

- small C
- medium C
- large C

Varying the capacitance C will only vary the time-delay.



ie It does not have any bearing on the current.

(Only the Resistance can vary the current in a dc circuit)

From  $t = RC \therefore t \propto C$

ie The greater the capacitance the greater the time-delay.

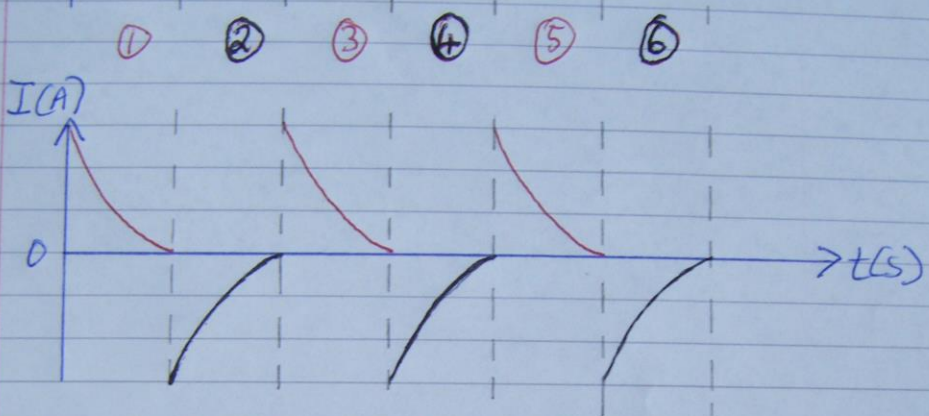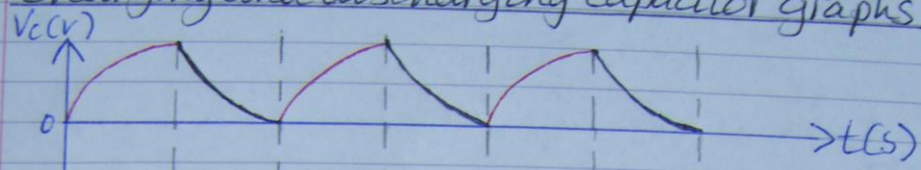
# Charging and discharging capacitor graphs



KEY ①, ③ and ⑤ ⇒ Charging cycles  
 ②, ④ and ⑥ ⇒ discharging cycles.

Why does the current start at a negative maximum in the discharge cycle?

EX6 (A/B STANDARD IN EXAM!!)

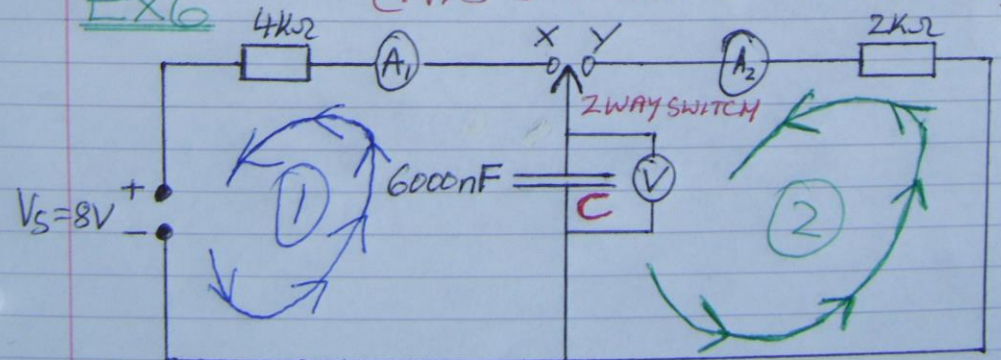

The 2 way switch can either go to contact X or contact Y.

(14)

When connected to X  $\Rightarrow$  Charging cycle

When connected to Y  $\Rightarrow$  discharging cycle

Q+A Calculate or find:

a) i) max reading on  $(A_1)$  during the charging cycle.

$$I = \frac{V_R}{R} = \frac{8}{4 \times 10^3} = \underline{2 \times 10^{-3} \text{ A}}$$

ii) max reading on  $(A_2)$  during the discharging cycle.

$$I = \frac{V_R}{R} = \frac{8}{2 \times 10^3} = \underline{4 \times 10^{-3} \text{ A}}$$

b) Charge stored on the capacitor when fully charged.

$$Q = ?$$

$$V = 8 \text{ V}$$

$$C = 60000 \text{ nF} = 60000 \times 10^{-9} \text{ F}$$

$$Q = VC$$

$$\Rightarrow Q = 8 \times 60000 \times 10^{-9}$$

$$\Rightarrow \underline{Q = 4.8 \times 10^{-5} \text{ C}}$$

c) Energy stored on the capacitor when fully charged.

$$\textcircled{1} E_{\text{CAP}} = \frac{1}{2} QV$$
$$= \frac{1}{2} \times 4.8 \times 10^{-5} \times 8$$

$$\underline{E_{\text{CAP}} = 1.92 \times 10^{-4} \text{ J}}$$

$$\text{OR } E_{\text{CAP}} = \frac{1}{2} CV^2$$

$$\Rightarrow E_{\text{CAP}} = \frac{1}{2} \times 60000 \times 10^{-9} \times 8^2$$

$$\Rightarrow \underline{E_{\text{CAP}} = 1.92 \times 10^{-4} \text{ J}}$$


d) The capacitor takes 12 seconds to fully charge up. The capacitor then takes a further period of time to then discharge.

Draw a graph with readings to show  $V_c$  against time for the 12s charging period and the discharging period thereafter.

charging cycle  $\Rightarrow R = 4k\Omega$  and time = 12s


Discharging cycle  $\Rightarrow R = 2k\Omega \therefore$  time = 6s.

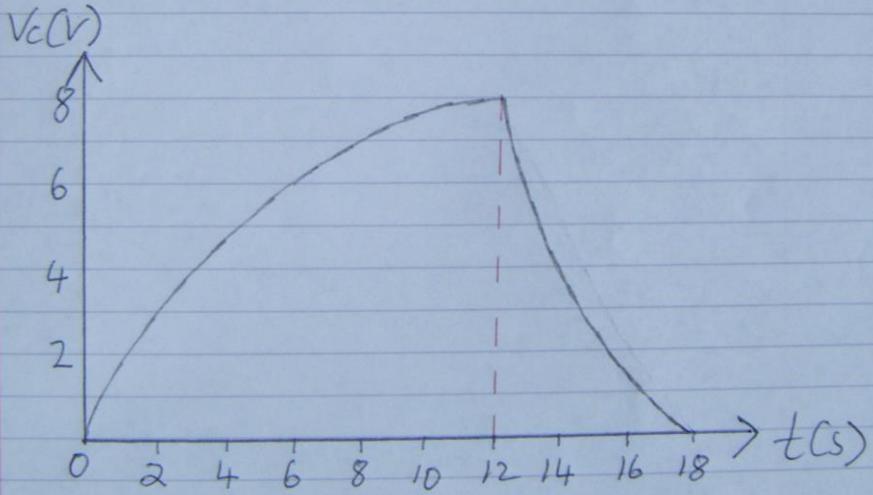Why 6s?  $t = RC \Rightarrow t \propto R$ .



0  $\rightarrow$  12s  $\Rightarrow$  charging

12  $\rightarrow$  18s  $\Rightarrow$  discharging.

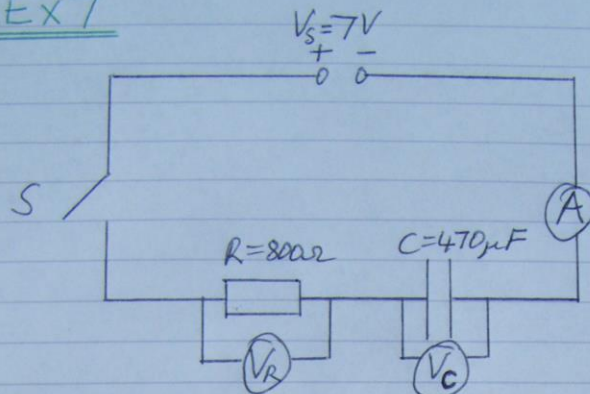Ex 7

C is initially uncharged and starts to charge when S is closed.

Calculate or find:

- a) The max reading on  $\text{A}$  when S is closed. (at that instant)

$$I = \frac{V_R}{R} = \frac{7}{800} = \underline{\underline{8.75 \times 10^{-3} \text{ A}}}$$

- b) Suggest a suitable range for the ammeter.

$$I_{\text{max}} = 8.75 \times 10^{-3} \text{ A} = 8.75 \text{ mA} \therefore \text{Range D} \rightarrow 10 \text{ mA}$$

- c) When  $V_C = 2.5 \text{ V}$  during the charging process then what is the reading on the ammeter at this instant?

$$I = \frac{V_R}{R} = \frac{7 - 2.5}{800} = \frac{4.5}{800} = \underline{\underline{5.63 \times 10^{-3} \text{ A}}}$$

- d) Calculate the energy stored in the capacitor when it is fully charged.

$$E_{\text{CAP}} = \frac{1}{2} C V^2 = \frac{1}{2} \times 470 \times 10^{-6} \times 7^2$$

$$\Rightarrow \underline{\underline{E_{\text{CAP}} = 1.15 \times 10^{-2} \text{ J}}}$$



(17)

- e) Calculate the charge stored on the capacitor when it is fully charged.

$$Q = VC = 7 \times 470 \times 10^{-6} = \underline{\underline{3.29 \times 10^{-3} \text{ C}}}$$

- f) What effect will increasing the resistance from  $800 \Omega$  to  $1 \text{ k}\Omega$  have in terms of:


- i)  $I_{\text{max}}$ , the maximum current
- ii) Time to charge up the capacitor.

i) As  $R \uparrow \therefore I_{\text{max}} \downarrow$


ii) From  $t = RC$  as  $R \uparrow \therefore t \uparrow$  ( $t = RC$ )  
 $t \propto R$

## A Resistive ac circuit

(18)

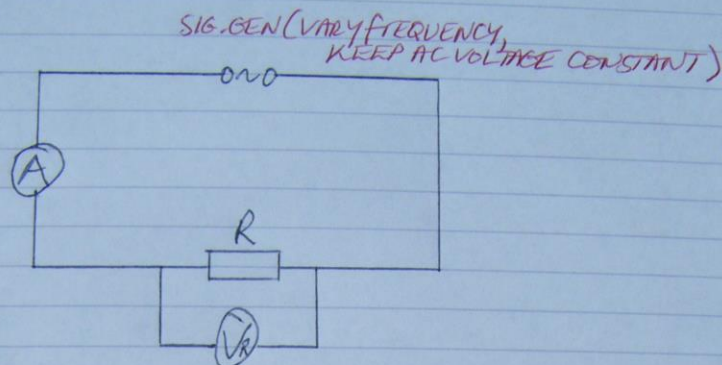

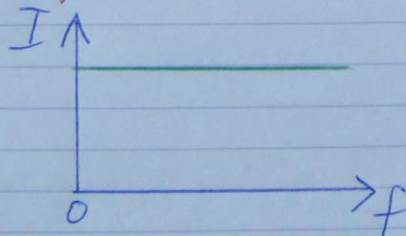- The frequency from the sig. gen is varied from 200Hz to 600Hz.
- The corresponding ac currents are taken from the  $\text{A}$  for each of the frequencies.
- The voltage across the resistor must be kept constant ( $\approx 2\text{V}$ ) throughout the experiment.
- Graph of  $I$  v  $f$




### Conclusion


The current stays constant when the frequency is varied in an ac Resistive Circuit.

## A capacitive ac circuit

(19)

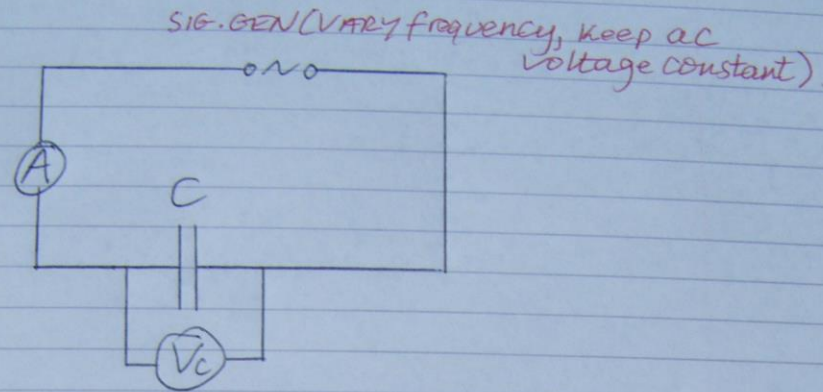

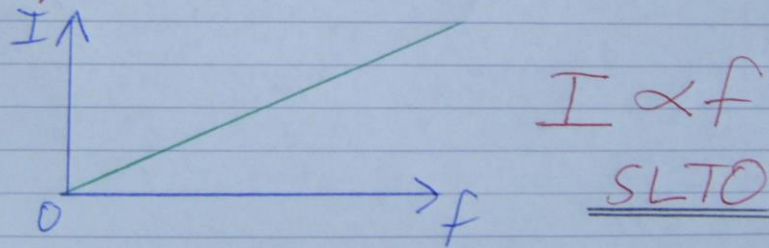- The same three steps as used in the ac resistive circuit.
- Graph of  $I$  v  $f$



- Conclusion  
As the frequency increases the ac current will also increase in direct proportion.  
This can be shown in the  $I$  v  $f$  graph which shows an SLTO.

NB One or both of these graphs will come up in the exam - 100% certainty!!