

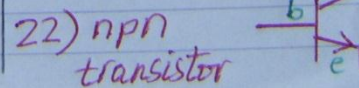
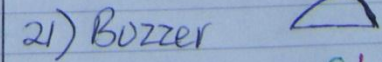
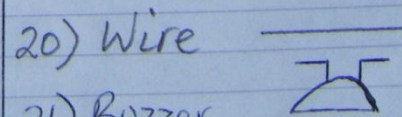
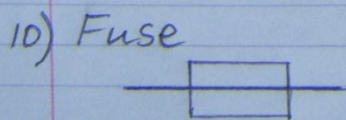
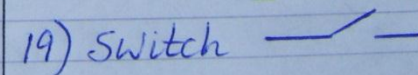
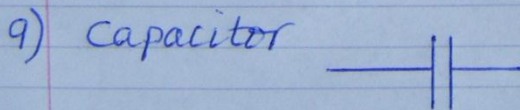
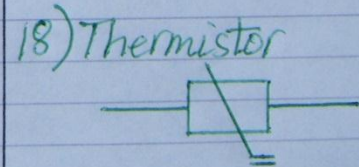
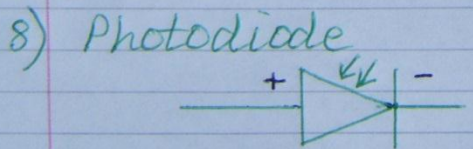
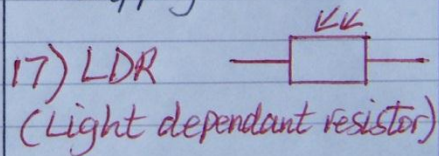
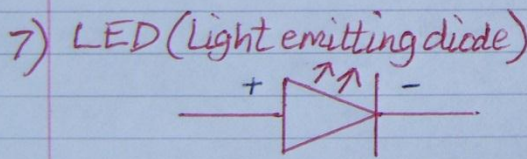
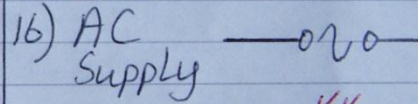
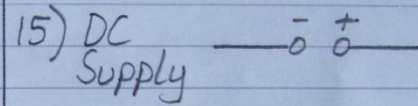
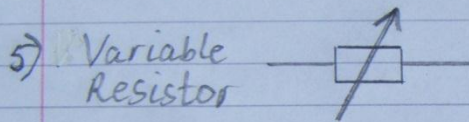
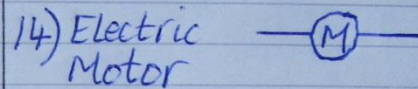
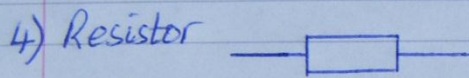
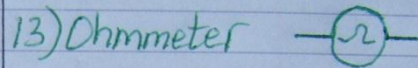
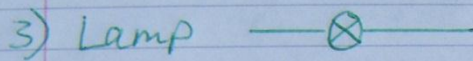
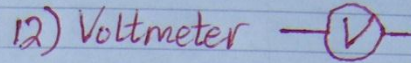
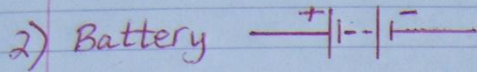


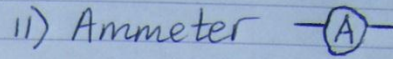

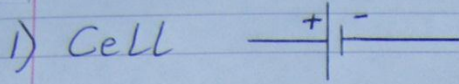Electrical Circuits - B M C M U L L E N ^①



(2)

Resistors

These are components which oppose the flow of current in an electrical circuit.

ie Resistance \downarrow \therefore Current \uparrow and
Resistance \uparrow \therefore Current \downarrow

This can be described using the defence of a football team.

If a team has a good defence then they will not concede many goals

ie Resistance \uparrow \therefore Current \downarrow

If a team has a very poor defence then they concede a lot of goals.

ie Resistance \downarrow \therefore Current \uparrow

(Current is related to the number of goals scored here!!)

Resistance Networks

Resistance is measured in the unit Ohms (Ω).

Resistors can be connected in :

- Series
- Parallel
- combination of series and parallel.

(3)


Resistors in series

The resistors are connected in line with one another. This allows only one path for the current to take.

$$* R_s = R_1 + R_2 + R_3 + \dots *$$

As more resistors are added in series the total resistance in series increases.


Ex 1

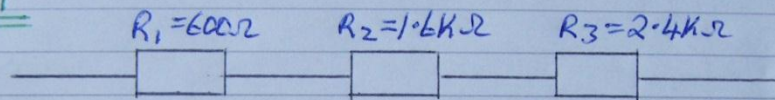

$$R_s = R_1 + R_2 + R_3 = 600 + 1600 + 2400$$

$$\Rightarrow \underline{R_s = 4600\Omega} \quad (\text{All resistors are converted to } \Omega \text{ or } k\Omega)$$

Ex 2

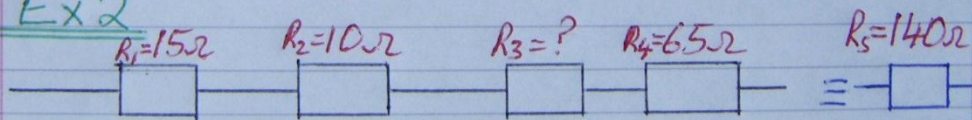

$$R_s = R_1 + R_2 + R_3 + R_4$$

$$\Rightarrow 140 = 15 + 10 + R_3 + 65$$

$$\Rightarrow 140 = 90 + R_3$$

$$\Rightarrow R_3 = 140 - 90 = \underline{50\Omega}$$


• Resistors in parallel.

The resistors are connected across one another. This allows more than one path for the current to take.

* $\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$ *

As more resistors are added in parallel then the total resistance in parallel decreases.


Ex 3

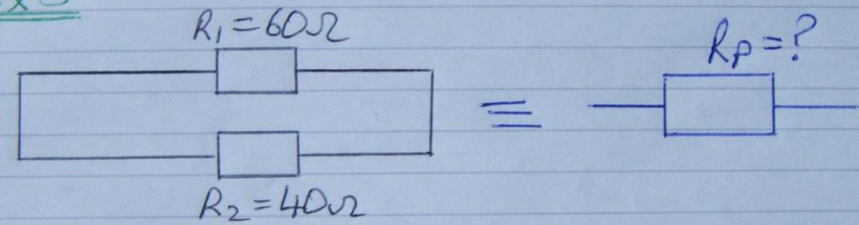

$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} \Rightarrow \frac{1}{R_p} = \frac{1}{60} + \frac{1}{40} = 60^{-1} + 40^{-1}$

$\Rightarrow \frac{1}{R_p} = \frac{1}{24} \Rightarrow R_p = 24 \Rightarrow \underline{\underline{R_p = 24\Omega}}$

Ex 4

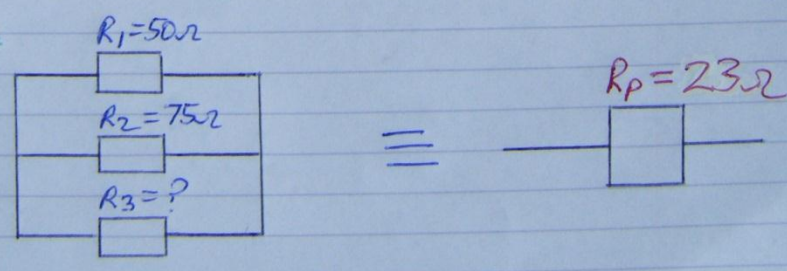

(5)

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\Rightarrow \frac{1}{23} = \frac{1}{50} + \frac{1}{75} + \frac{1}{R_3} \Rightarrow \frac{1}{R_3} = \frac{1}{23} - \frac{1}{50} - \frac{1}{75}$$

$$\Rightarrow \frac{1}{R_3} = 23^{-1} - 50^{-1} - 75^{-1} = \frac{7}{690}$$

$$\Rightarrow \frac{R_3}{1} = \frac{690}{7} \Rightarrow \underline{\underline{R_3 = 98.6 \Omega}}$$

* The total resistance in a parallel resistance network is smaller than the lowest resistance in parallel.


∴ Before attempting EX3 which had a 60Ω and 40Ω resistors in parallel, we could conclude that the total resistance in parallel would be less than 40Ω . *

• Combination of Series + Parallel Resistors
The total resistance in a network which involves resistors in series and parallel connected together would be:

$$* R_T = R_s + R_p *$$


$$R_s = R_1 + R_4$$
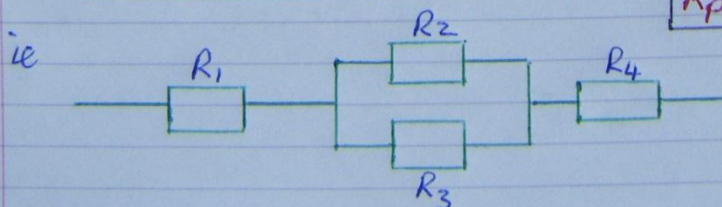
$$\frac{1}{R_p} = \frac{1}{R_2} + \frac{1}{R_3}$$



⑥

EX5

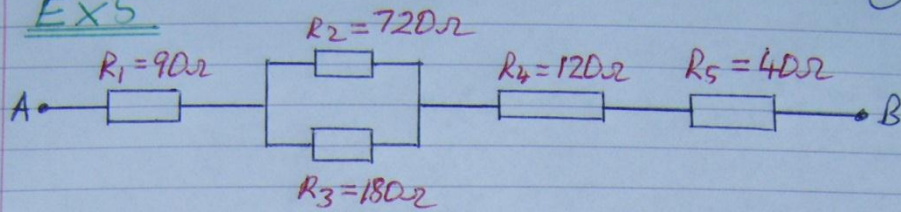

Calculate the total resistance between A and B.


- $R_s = R_1 + R_4 + R_5 = 90 + 120 + 40 = \underline{\underline{250\Omega}}$

- $\frac{1}{R_p} = \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{720} + \frac{1}{180}$

- $\Rightarrow \frac{1}{R_p} = \frac{1}{144} \Rightarrow \frac{R_p}{1} = \frac{144}{1} \Rightarrow \underline{\underline{R_p = 144\Omega}}$

- $R_T = R_s + R_p = 250 + 144 = \underline{\underline{394\Omega}}$

EX6

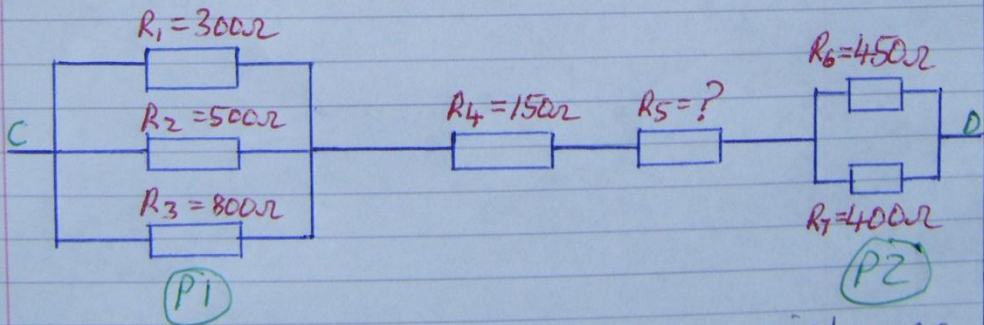

Calculate the unknown resistance R_5 if the total resistance in the network $R_T = 600\Omega$ between C and D.

(7)

$$\bullet R_s = R_4 + R_5 = \underline{(150 + R_5)} \Omega$$

$$\bullet \textcircled{P1} \quad \frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{300} + \frac{1}{500} + \frac{1}{800}$$

$$\Rightarrow \frac{1}{R_p} = 300^{-1} + 500^{-1} + 800^{-1} = \frac{79}{12000}$$

$$\Rightarrow \frac{R_p}{1} = \frac{12000}{79} \Rightarrow \underline{R_p = 152 \Omega}$$

$$\bullet \textcircled{P2} \quad \frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{450} + \frac{1}{400}$$

$$\Rightarrow \frac{1}{R_p} = 450^{-1} + 400^{-1} = \frac{17}{3600}$$

$$\Rightarrow \frac{R_p}{1} = \frac{3600}{17} \Rightarrow \underline{R_p = 212 \Omega}$$

$$\bullet R_T = R_s + R_p = R_s + \textcircled{P1} + \textcircled{P2}$$


$$\Rightarrow 600 = (150 + R_s) + 152 + 212$$

$$\Rightarrow 600 = 514 + R_s$$

$$\Rightarrow R_s = 600 - 514 = 86$$


$$\Rightarrow \underline{R_s = 86 \Omega}$$

Ex7

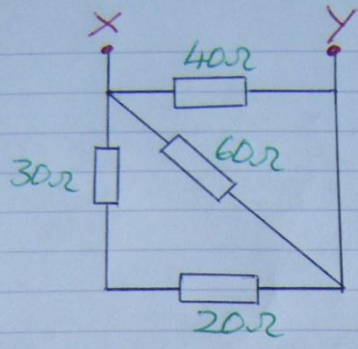

Calculate the resistance between X and Y in the network.

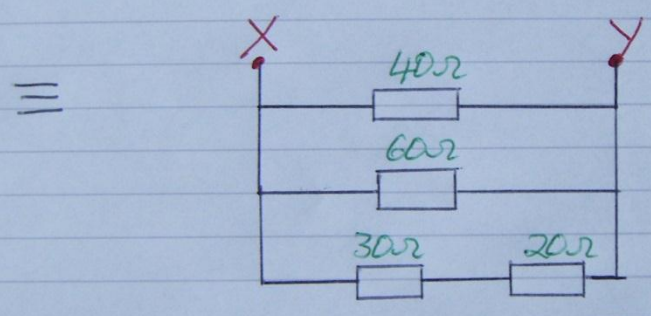- Redraw the diagram to make it easier to read. (Think of the possible paths that the current needs to take to go from X to Y.)




As the 30Ω and 20Ω resistors are in series with each other then this would add up to 50Ω in the third branch in parallel.

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{40} + \frac{1}{60} + \frac{1}{50}$$

$$\Rightarrow \frac{1}{R_p} = 40^{-1} + 60^{-1} + 50^{-1} = \frac{37}{600}$$

$$\Rightarrow \frac{R_p}{1} = \frac{600}{37} \Rightarrow \underline{\underline{R_p = R_{xy} = 16.2 \Omega}}$$

Series Circuits

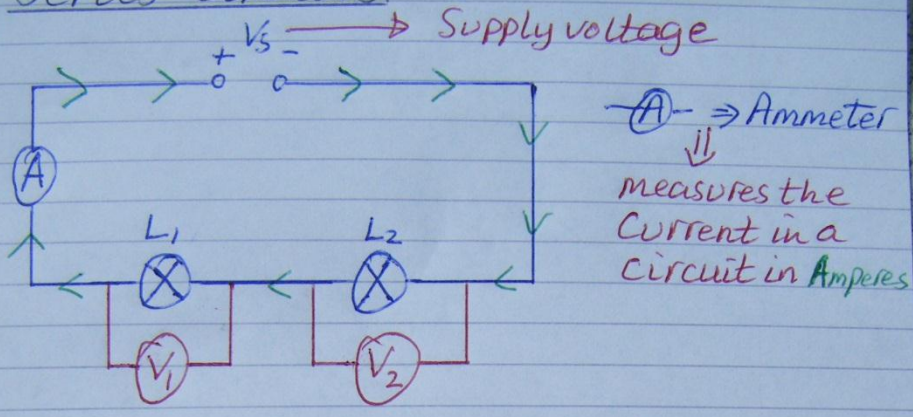

ⓐ ⇒ Ammeter
 ↓
 measures the current in a circuit in Amperes

Ⓥ ⇒ Voltmeter
 ↓
 measures the voltage across a component in Volts.

- Ammeters are connected in a circuit in series.
- Voltmeters are connected in a circuit in parallel.

* Current passes through components in a circuit.


Voltage is dropped across components in a circuit. *

- In a series circuit the current is the same at any point in the circuit
- In a series circuit the supply voltage is split up between the components in the circuit.

$$V_s = V_1 + V_2 + \dots$$

Parallel Circuits

(11)

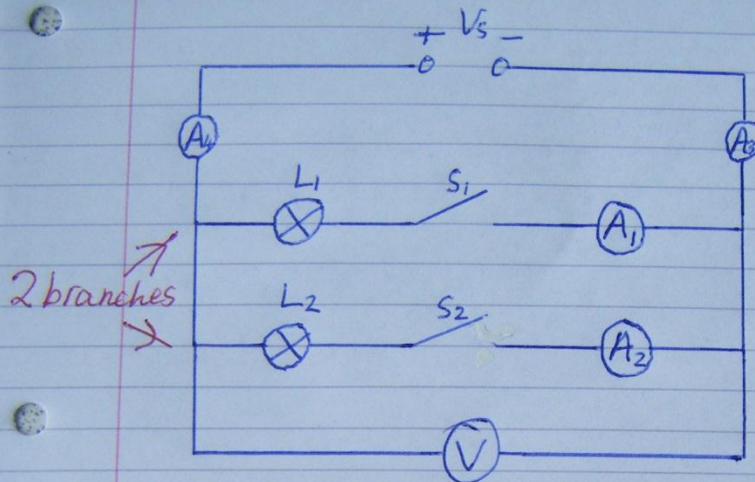

If each of the switches are closed then:

- Current splits up in a parallel circuit between its branches.

$$\text{ie } \text{---} A_4 \text{---} \text{ or } \text{---} A_3 \text{---} = \text{---} A_1 \text{---} + \text{---} A_2 \text{---}$$


- Voltage dropped across each branch in a parallel circuit is the same.
- In a purely parallel circuit the voltage dropped across each component is the same as the supply voltage.

Ohms Law

This links Voltage, Current and Resistance.

$$V = I \times R$$

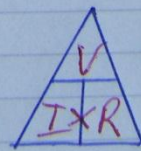↓ Voltage (V)
↓ current (A)
→ Resistance (R)




1. $V = IR$

2. $I = \frac{V}{R}$

3. $R = \frac{V}{I}$

Using a multimeter to measure Current, Voltage and Resistance

*

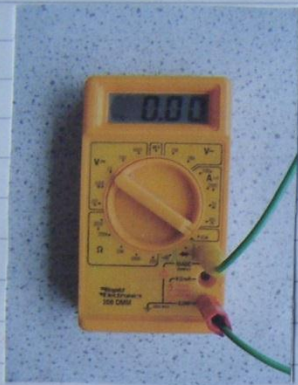

DC CURRENT


TERMINALS

- COM
- 10A DC

RANGE SCALE

- 10A ===

*

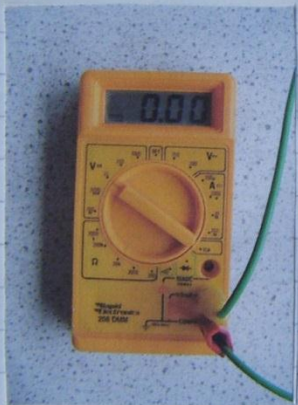

DC VOLTAGE


TERMINALS

- COM
- VΩ mA

RANGE SCALE

- 20V ===

*

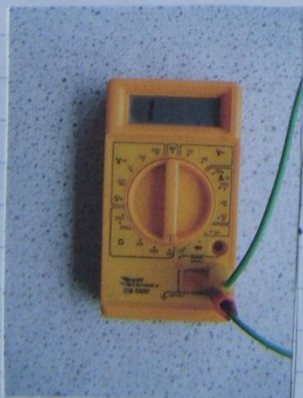

RESISTANCE

TERMINALS

- COM
- VΩ mA

RANGE SCALE

- 200Ω (OR HIGHER!!)

(13)

Voltage Dividers

In a series circuit we talked about the current being the same at any point in the circuit.

From Ohms Law $I = \frac{V}{R}$ then

$$I = \frac{V_1}{R_1} \text{ or } I = \frac{V_2}{R_2}$$

ie The ratio of Voltage drop to resistance will be the same across any component.

$$\therefore \boxed{\frac{V_1}{R_1} = \frac{V_2}{R_2}}$$

Compare Mr McMullen to a first year boy.


Mr McMullen is much bigger and uglier than the first year boy.
Mr McMullen will also eat far more than the first year boy.

Conclusion

- Resistance is linked with the size of the person
- Voltage is linked with how much food they eat.

This is discussed very loosely but I hope that it gets the point across.

Voltage Divider Circuits

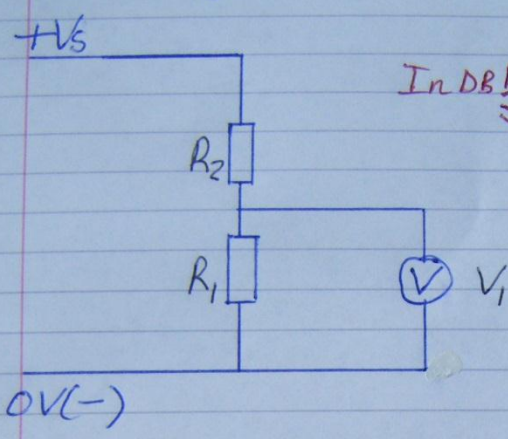


Bear Equation
In DB!!!

$$V_1 = \left(\frac{R_1}{R_1 + R_2} \right) \times V_s$$

Also

$$V_2 = \left(\frac{R_2}{R_1 + R_2} \right) \times V_s$$

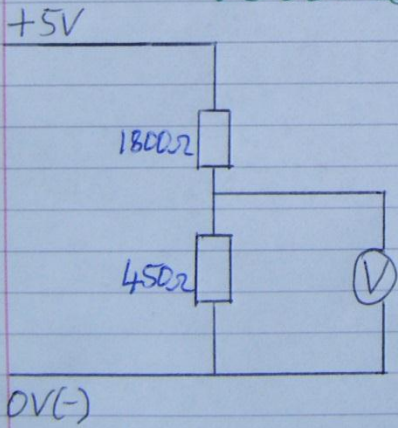Ex 8 Calculate the reading on the voltmeter $\text{---} \text{V} \text{---}$.



$$V_1 = \left(\frac{R_1}{R_1 + R_2} \right) \times V_s$$

$$\Rightarrow V_1 = \left(\frac{450}{450 + 1800} \right) \times 5V$$


$$\Rightarrow V_1 = \frac{450}{2250} \times 5V$$

$$\Rightarrow V_1 = \frac{1}{5} \times 5V = \underline{\underline{1V}}$$

* $(\because V_{1800\Omega} = 5V - 1V = 4V)$ *

* The resistance on the numerator of the 'Bear Equation' is the resistor that you are calculating the voltage dropped across it. *

Ex 9
+8V

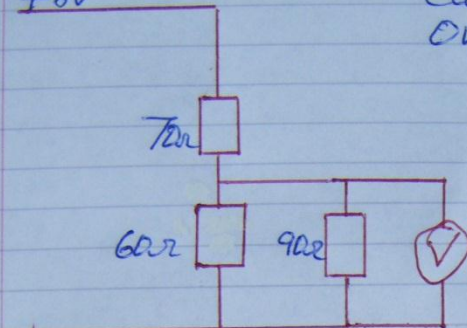

Calculate the reading on the voltmeter V_1 .


- Calculate the total resistance in parallel
- Then apply the 'Bear Equation'.

0V(-)

$$\bullet \frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{60} + \frac{1}{90}$$

$$\Rightarrow \frac{1}{R_p} = \frac{1}{36} \Rightarrow \frac{R_p}{1} = \frac{36}{1} \Rightarrow \underline{R_p = 36\Omega}$$

+8V (Simplified Circuit diagram)

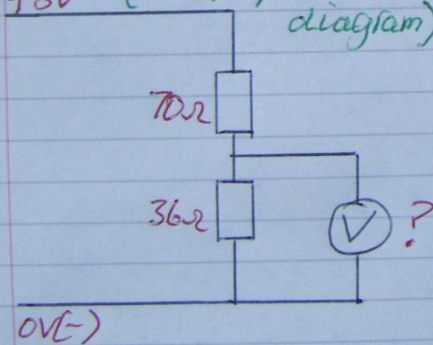

• 'Bear Equation'

$$V_1 = \left(\frac{R_1}{R_1 + R_2} \right) \times V_s$$

$$\Rightarrow V_1 = \left(\frac{36}{36 + 70} \right) \times 8V$$


$$\Rightarrow V_1 = \frac{36 \times 8V}{106} = \underline{2.72V}$$

(The voltage across the 70Ω resistor would be $8V - 2.72V = \underline{5.28V}$)

CIRCUIT NETWORK PROBLEMS

(16)


Ex 10

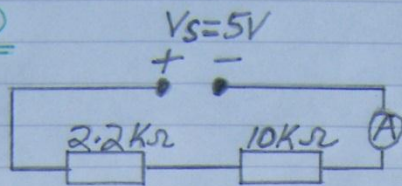

Calculate the reading on the ammeter A in mA.

- $R_s = R_1 + R_2 = 2200 + 10,000 = 12,200\Omega$
- $V = IR \Rightarrow I = \frac{V}{R} = \frac{5}{12200} = \underline{4.1 \times 10^{-4} A}$
- $4.1 \times 10^{-4} A = 0.41 \times 10^{-3} A = \underline{0.41 mA}$

Ex 11

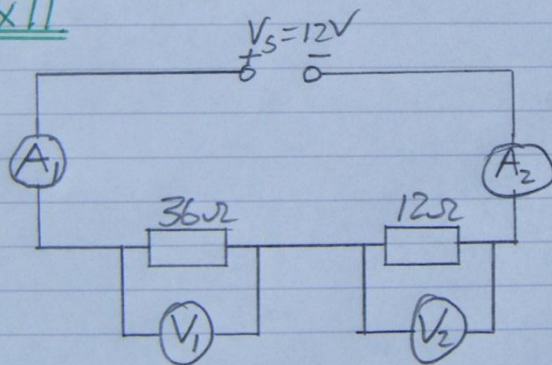

Calculate or find:

- a) Readings on
- i) A_1
 - ii) A_2
- b) Readings on
- i) V_1
 - ii) V_2

a) $R_s = R_1 + R_2 = 36 + 12 = \underline{48\Omega}$

i) + ii) $I = \frac{V}{R} = \frac{12}{48} = \underline{0.25A}$

{ Series Circuit
Current is the same!!


b) i) $V_1 = IR_1 = 0.25 \times 36 = \underline{9V}$

ii) $V_2 = IR_2 = 0.25 \times 12 = \underline{3V}$

(Check $V_s = V_1 + V_2 \Rightarrow 12V = 9V + 3V$) ✓

Ex 12

$V_s = 8V$

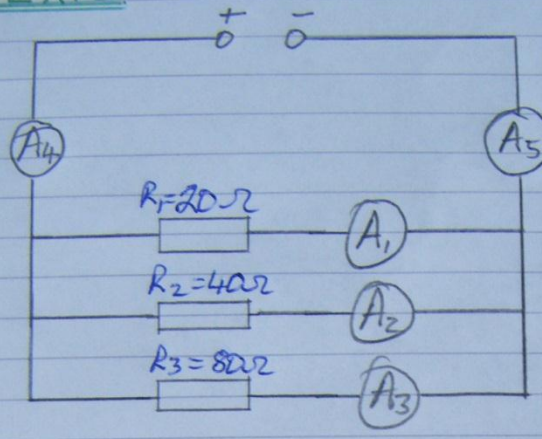

Calculate or find:
a) Total resistance

b) Readings on
i) A_4 ii) A_5

c) Readings on
i) A_1
ii) A_2
iii) A_3

A a) $\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{20} + \frac{1}{40} + \frac{1}{80}$

$\Rightarrow \frac{1}{R_p} = 20^{-1} + 40^{-1} + 80^{-1} \Rightarrow \frac{1}{R_p} = \frac{7}{80}$

$\Rightarrow \frac{R_p = 80}{1 \quad 7} \Rightarrow \underline{\underline{R_p = 11.4 \Omega}}$

b) A_4 and A_5 will be the same

$I = \frac{V}{R} = \frac{8}{11.4} = \underline{\underline{0.70A}}$

c) i) $I_1 = \frac{V}{R_1} = \frac{8}{20} = \underline{\underline{0.40A}}$

ii) $I_2 = \frac{V}{R_2} = \frac{8}{40} = \underline{\underline{0.20A}}$

iii) $I_3 = \frac{V}{R_3} = \frac{8}{80} = \underline{\underline{0.10A}}$


check!!

$I_T = I_1 + I_2 + I_3$

$\Rightarrow 0.70 = 0.40 + 0.20 + 0.10$

✓
check!!

(18)

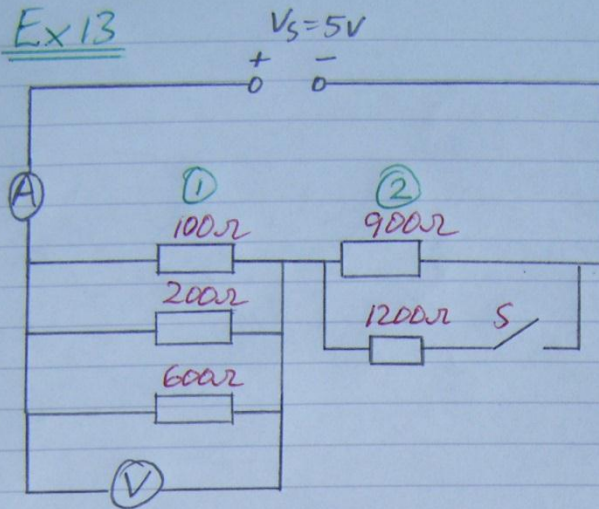Ex 13

Calculate or find:
The reading on

i) — (A) —

ii) — (V) —

when

a) switch S is open

b) switch S is closed.

A a) When S is open.

$$i) \cdot \frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{100} + \frac{1}{200} + \frac{1}{600}$$

$$\Rightarrow \frac{1}{R_p} = 100^{-1} + 200^{-1} + 600^{-1} = \frac{1}{60} \Rightarrow R_p = 60$$

$$\Rightarrow \underline{R_p = 60\Omega}$$

$$R_s = 900\Omega \quad \therefore R_T = R_s + R_p = 900 + 60 = \underline{960\Omega}$$

$$I = \frac{V_s}{R_T} = \frac{5}{960} = \underline{5.21 \times 10^{-3} A}$$

$$ii) \quad V = IR = 5.21 \times 10^{-3} \times 60 = \underline{0.31V}$$

↑

The voltmeter is placed across the parallel combination $\equiv 60\Omega$ in series.

b) When S is closed

1) • The 900Ω and 1200Ω resistors are now connected in parallel.

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{900} + \frac{1}{1200} = 900^{-1} + 1200^{-1}$$

$$\Rightarrow \frac{1}{R_p} = \frac{7}{3600} \Rightarrow \frac{R_p}{1} = \frac{3600}{7} \Rightarrow \underline{R_p = 514\Omega}$$


$$R_T = R_p \textcircled{1} + R_p \textcircled{2} = 60 + 514 = \underline{574\Omega}$$

$$I = \frac{V_s}{R_T} = \frac{5}{574} = \underline{8.71 \times 10^{-3} A}$$

$$ii) V = IR = 8.71 \times 10^{-3} \times 60 = \underline{0.52V}$$

Again the voltmeter is placed across the 100Ω, 200Ω and 600Ω parallel combination
≡ 60Ω in series.

Ex 14

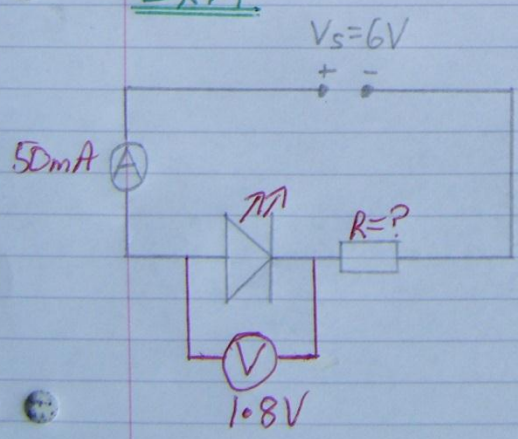

Calculate the unknown Resistance R.

$$\bullet V_R = 6V - 1.8V = \underline{4.2V}$$

$$\bullet R = \frac{V_R}{I} = \frac{4.2}{50 \times 10^{-3}} = \underline{84\Omega}$$

Electrical Power

Power is defined as the energy transformed per second.

$$P = \frac{E}{t}$$

Power (Watts) Energy (Joules) time (seconds)


1 Watt = 1 Joule per second

1W = 1Js⁻¹

Electrical Energy Equations.

- $P = IV$ V → Voltage
 - $P = I^2R$ I → Current
 - $P = \frac{V^2}{R}$ R → Resistance
- P → Power.

EX15

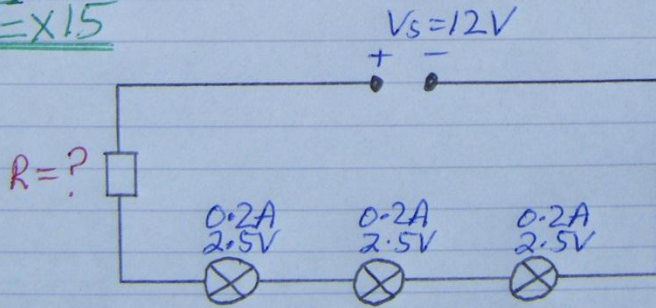

Calculate or find:
a) Power of the lamps

$$a) P = IV \Rightarrow P = 0.2 \times 2.5$$

$$\Rightarrow P = \underline{\underline{0.5W}}$$

b) The unknown Resistance R.

$$b) R = \frac{V_R}{I} = \frac{12 - 7.5}{0.2} = \underline{\underline{22.5\Omega}}$$