
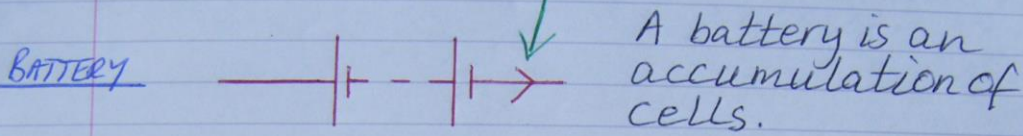


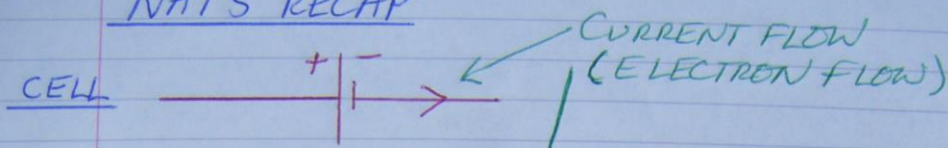


BMMULLEN ①

# HIGHER EMF AND INTERNAL RESISTANCE

## NATS RECAP



## In reality

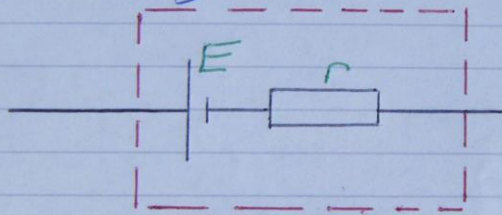

Everything inside the broken line box is within the battery.

$E$  = Emf of a battery or cell.


$r$  = Internal resistance of the battery or cell.

↑ must be written as a small case letter.


Capital  $R$  stands for the external resistance or the load resistance.

\* The emf of a battery never changes ie it has a constant reading. \*

eg! Smoke alarm batteries

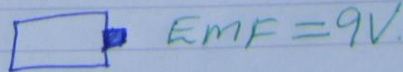

eg 2

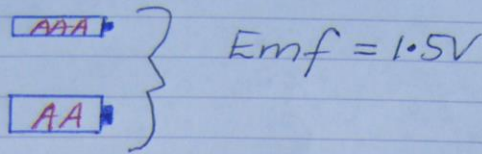


Internal resistance of a battery

- Brand new battery  $\Rightarrow r$  is low
- Old battery  $\Rightarrow r$  is high.

EQUATION

$$E = V + Ir$$

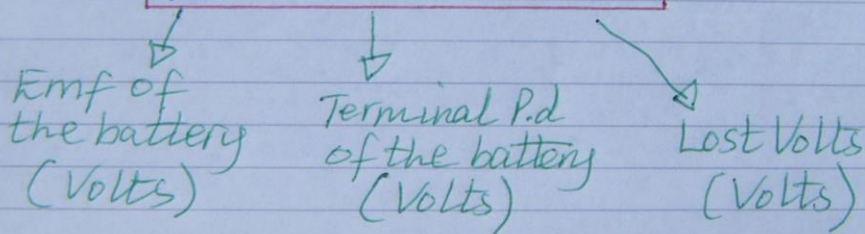

\* Lost Volts =  $Ir$  \*

$I$   $\swarrow$  Current  
 $r$   $\searrow$  Internal resistance.

- Emf is always constant
- New battery  $\Rightarrow r$  is low  $\Rightarrow$  lost volts is low.

If lost volts is low then terminal potential difference is high.

$\leftarrow$   $\uparrow$   $\downarrow$   
 $E = V + Ir$



③

- Old battery  $\Rightarrow r$  is high  $\Rightarrow$  lost volts is high

If lost volts is high then terminal potential difference is low.


$$E = V + Ir$$

### Definitions

- \* • Emf  $\rightarrow$  Electromotive force (volts)
  - $\rightarrow$  The energy given to each coulomb of charge as it passes through the source.
- \* • V  $\rightarrow$  Terminal potential difference (volts)
  - $\rightarrow$  This is the energy given to each coulomb of charge.
  - $\rightarrow$  This is the effective output voltage of a battery.
- \* • Ir  $\rightarrow$  lost volts (volts)
  - $\rightarrow$  The voltage dropped across the internal resistance of a battery.
- \* The difference in the definitions for Emf and  $V_{pd}$  is the last six words in the Emf definition \*

## The standard Emf Circuit

(4)

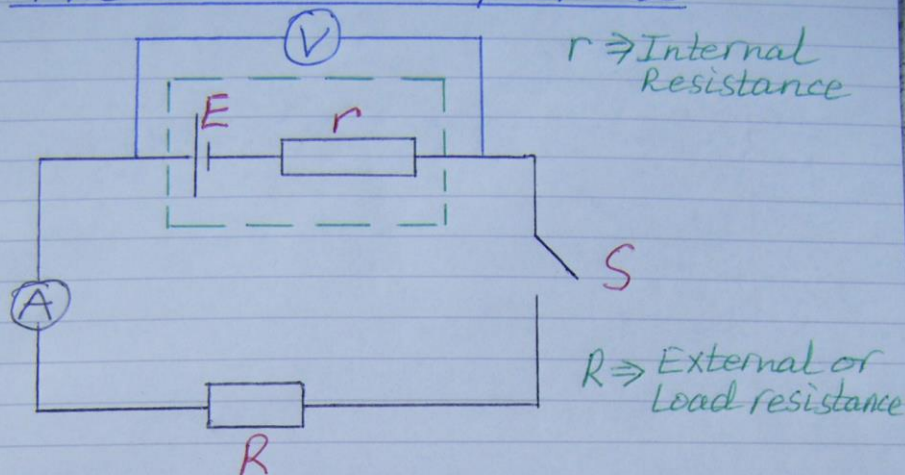

• Switch is open  $\Rightarrow$  Ammeter reading =  $0A$   
Voltmeter reading =  $Emf$

• Switch is closed  $\Rightarrow$  Ammeter reading  $> 0A$   
Voltmeter reading =  $V$

$$* \text{ Emf} > V *$$

Why?

As a current flows we now have a voltage dropped across the internal resistance i.e. lost volts

$$E = V + Ir$$

$\leftarrow \downarrow \uparrow$


As the terminal potential difference decreases the lost volts increases.



Three variations of the equations

- $E = V + Ir \Rightarrow$  In DB!!
- $E = IR + Ir \Rightarrow$  From  $V = IR$
- $E = I(R + r) \Rightarrow$  Taking I out as a common factor.

Ex 1

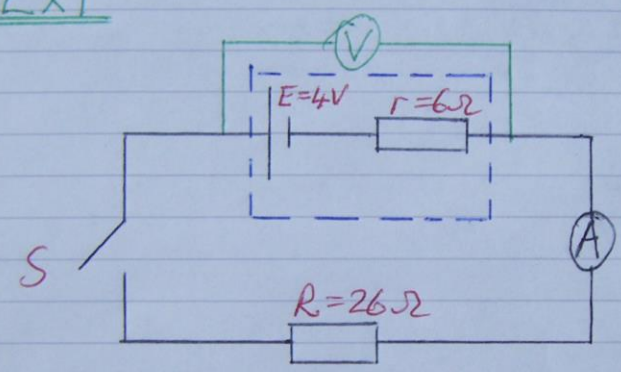

Q Calculate or find the following when the switch S is closed:

- Emf
- Reading on the  $\text{A}$
- Reading on the  $\text{V}$
- Explain why there is a difference between the readings in a) and c).

6

A) a) Emf is the reading on the  $\text{---}\text{V}\text{---}$  when the switch is open i.e. 4V as no current will flow.

b) S closed  $\Rightarrow$  Current flowing

$$E = 4V$$

$$V = ?$$

$$I = ?$$

$$r = 6\Omega$$

$$R = 26\Omega$$

$$E = V + Ir$$

$$\Rightarrow E = IR + Ir$$

$$\Rightarrow E = I(R + r)$$

$$\Rightarrow 4 = I(26 + 6)$$

$$\Rightarrow 32I = 4 \Rightarrow I = \frac{4}{32} = \underline{\underline{0.125A}}$$

c) OPTION 1

OR

OPTION 2

$$V = IR$$

$$\Rightarrow V = 0.125 \times 26$$

$$\Rightarrow \underline{\underline{V = 3.25V}}$$

$$E = V + Ir$$

$$\Rightarrow 4 = V + 0.125 \times 6$$

$$\Rightarrow 4 = V + 0.75$$

$$\Rightarrow \underline{\underline{V = 3.25V}}$$

d) a) Emf = 4V

c)  $V_{\text{tpd}} = 3.25V$


- Emf  $\Rightarrow$  switch open  $\Rightarrow$  no current flows
- $V_{\text{tpd}}$   $\Rightarrow$  switch closed  $\Rightarrow$  current flows

$\therefore$  We now have to take internal resistance  $r$  and lost volts  $Ir$  into consideration.



Ex2

7

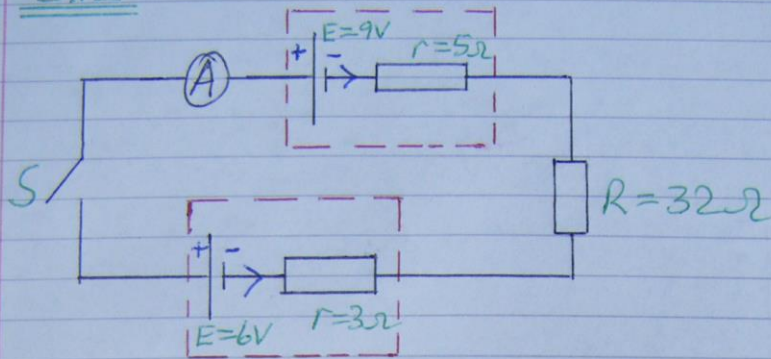

Q Calculate or find the following when the switch in the circuit is closed:

- a) The effective emf
- b) The total internal resistance
- c) The reading on the ~~A~~
- d) The terminal potential difference,  $V_{\text{tpd}}$

A a) Effective emf =  $9V - 6V = 3V$  (check polarity!!)


b)  $r_T = 5 + 3 = 8\Omega$

c)  $E = 3V$        $E = V + Ir \Rightarrow E = I(R + r)$   
 $R = 32\Omega$        $\Rightarrow 3 = I(32 + 8)$   
 $r = 8\Omega$        $\Rightarrow I = \frac{3}{40} = 0.075A$   
 $I = ?$

d)  $V = IR = 0.075 \times 32 = 2.4V$   
(could also use  $E = V + Ir$  for this part)

Ex 3

8

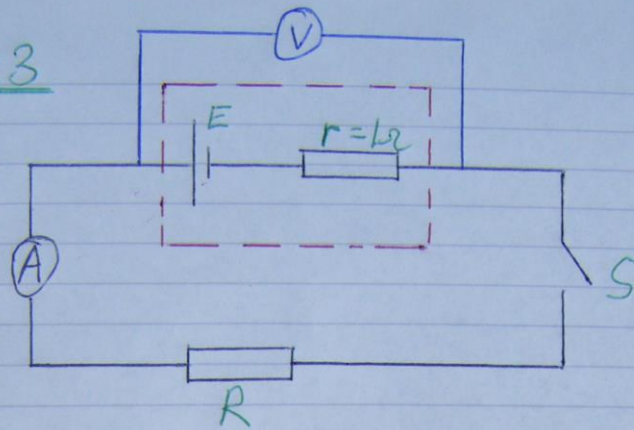

Readings on  $\text{---}\text{V}\text{---}$

•  $S$  is open  $\Rightarrow \text{---}\text{V}\text{---} = 12\text{V}$

•  $S$  is closed  $\Rightarrow \text{---}\text{V}\text{---} = 10.5\text{V}$

Q Calculate or find:

a) Emf of the cell. ( $E$ )

b) Terminal potential difference ( $V$ )

c) The reading on the ammeter when:  
i)  $S$  is open  
ii)  $S$  is closed.

d) External Load resistance ( $R$ ).

A a) Emf,  $E = 12\text{V}$


b)  $V_{\text{tpd}}$ ,  $V = 10.5\text{V}$

c) i)  $S$  open  $\Rightarrow$   $I = 0$ .



$$\begin{array}{ll}
 \text{c) ii) } E = 12\text{V} & E = V + Ir \\
 V = 10.5\text{V} & \Rightarrow 12 = 10.5 + I \times 1 \\
 r = 1\Omega & \Rightarrow I = \frac{12 - 10.5}{1} \\
 I = ? & \Rightarrow \underline{I = 1.5\text{A}}
 \end{array}$$

$$\begin{array}{l}
 \text{d) } R = ? \quad V = IR \\
 \Rightarrow R = \frac{V}{I} = \frac{10.5}{1.5} = \underline{7\Omega}
 \end{array}$$

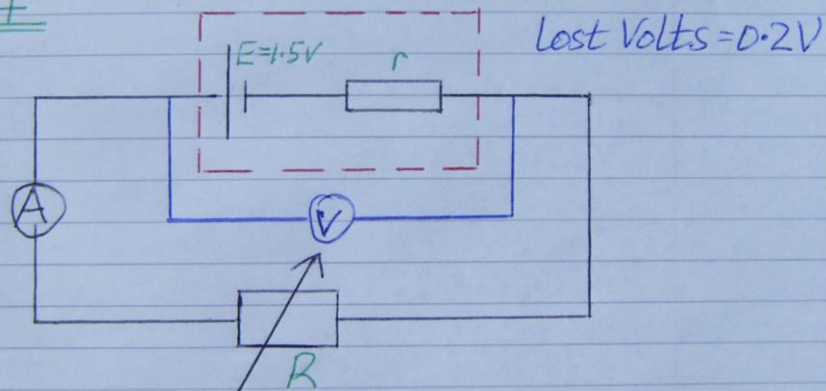Ex4

- Q
- Calculate the terminal potential difference across the cell.
  - Will the current increase or decrease as  $R$  is increased?
  - Explain what happens to the reading on the voltmeter when  $R$  is increased.

• A a)  $E = V + Ir \Rightarrow 1.5 = V + 0.2$   
 $\Rightarrow V = 1.5 - 0.2 = \underline{1.3V}$

b) As Resistance  $R \uparrow$  then the current  $I \downarrow$ .

c) • As the resistance  $\uparrow \therefore$  Current  $\downarrow$

• As current  $\downarrow \therefore$  Lost Volts  $= Ir \downarrow$


• As lost Volts  $= Ir \downarrow \therefore$  Terminal Pd,  $V \uparrow$

IMPORTANT  $\Rightarrow E = V + Ir$

• The terminal Pd,  $V$  is the voltage

• dropped across the variable resistor  $R. \therefore \uparrow$

Ex5

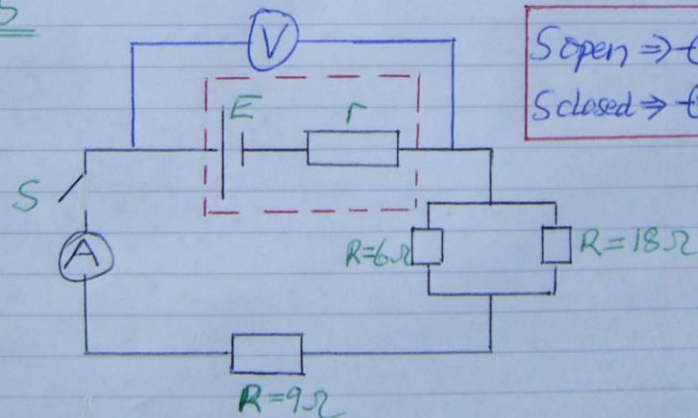

Open  $\Rightarrow V = 5.6V$

closed  $\Rightarrow V = 4.6V$

Q Calculate or find:

- Emf
- Terminal potential difference
- lost volts
- Internal resistance.



a)  $\text{Emf} = 5.6\text{V}$       c)  $\text{Lost Volts} = \text{Emf} - V_{\text{tpd}}$   
 $= 5.6 - 4.6$   
 $= \underline{1\text{V}}$

b)  $V_{\text{tpd}} = 4.6\text{V}$

d)  $r = ?$        $R_T = R_p + R_s$   
 $R = ?$

•  $R_p$ :  $\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{6} + \frac{1}{18}$

$\Rightarrow \frac{1}{R_p} = \frac{2}{9} \Rightarrow \frac{R_p}{1} = \frac{9}{2} \Rightarrow \underline{R_p = 4.5\Omega}$

•  $R_T$ :  $R_T = R_p + R_s = 4.5\Omega + 9\Omega = \underline{13.5\Omega}$

•  $E = V + Ir$       •  $V = IR \Rightarrow I = \frac{V}{R}$

$\Rightarrow 5.6 = 4.6 + 0.34r$


$\Rightarrow I = \frac{4.6}{13.5} = \underline{0.34\text{A}}$

$\Rightarrow 0.34r = 5.6 - 4.6$

$\Rightarrow 0.34r = 1$

$\Rightarrow r = \frac{1}{0.34} = \underline{3\Omega}$


### Short Circuits

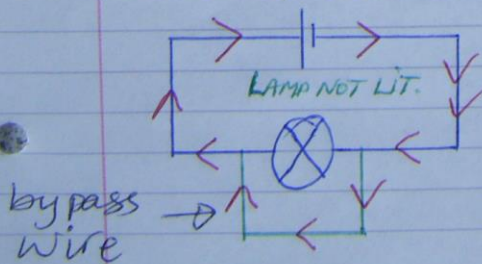

A lamp is a resistor that gives off light. A bypass wire placed around the lamp will take the current with none going through the lamp i.e. current follows the path of least resistance.

Ex 6

(12)

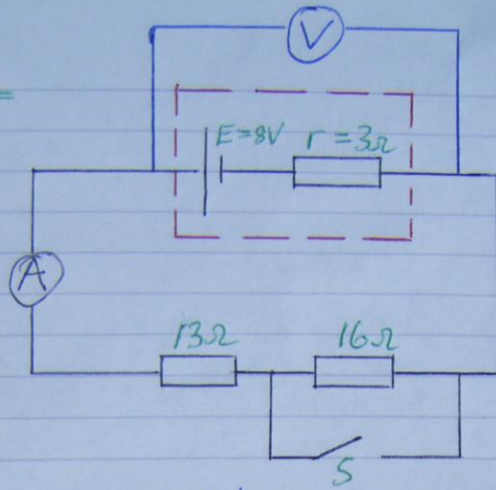

Q Calculate or find:

- a) Reading on  $\text{A}$  when
- i) S is open
  - ii) S is closed

- b) Reading on  $\text{V}$  when
- i) S is open
  - ii) S is closed.

When S is closed the 16Ω resistor is short circuited from the circuit  
XXXXXXXXXX

A a) i) S open  $\Rightarrow R = 13 + 16 = 29\Omega$   $E = I(R+r)$   
 $r = 3\Omega$   $\Rightarrow 8 = I(29+3)$   
 $E = 8V$   $\Rightarrow 32I = 8$   
 $\Rightarrow I = \frac{8}{32} = \underline{\underline{0.25A}}$

ii) S closed  $E = I(R+r)$   
 $\Rightarrow 8 = I(13+3)$   $\Rightarrow 16I = 8$   
 $\Rightarrow I = \frac{8}{16} = \underline{\underline{0.5A}}$

b) i) S open  $\Rightarrow V = IR = 0.25 \times 29 = \underline{\underline{7.25V}}$

ii) S closed  $\Rightarrow V = IR = 0.5 \times 13 = \underline{\underline{6.5V}}$




Ex7

Q

Voltage (V)	9	8	6	4	2
Current (A)	1	2	4	6	8

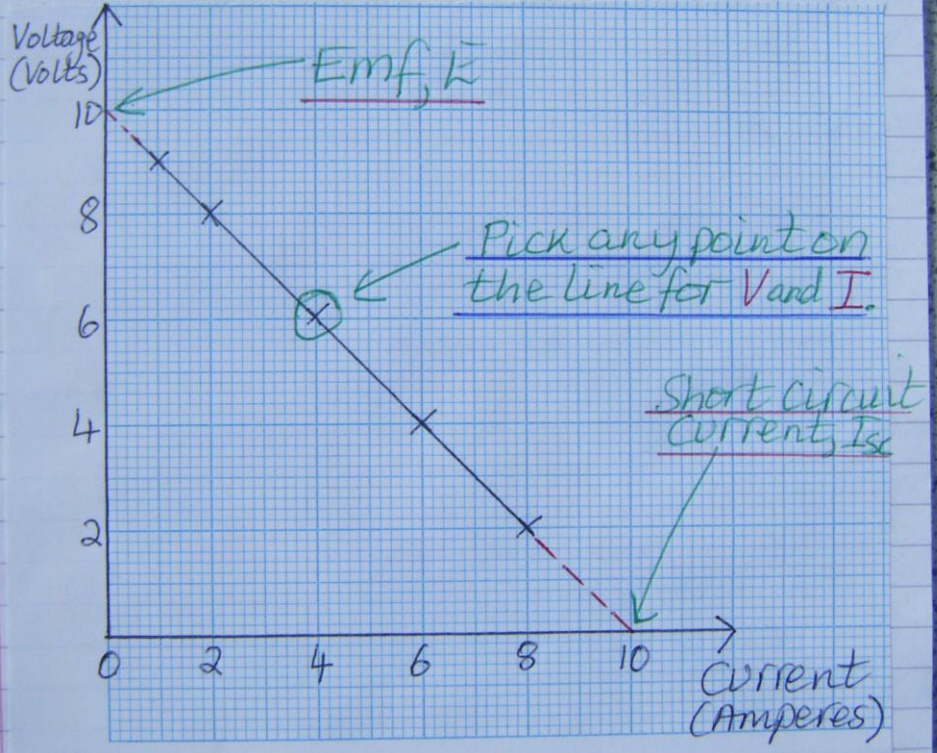a) Draw a line graph of Voltage (V) against current (A).



b) From the graph, calculate or find:

- i) Emf,  $E$
- ii) Internal Resistance,  $r$
- iii) Short circuit current,  $I_{sc}$



• A b) i) Emf,  $E$  when  $I=0$  is when the line cuts the y-axis.  
Emf = 10V

ii) Take one point (any) from the line and substitute this into  $E = V + Ir$  to find  $r$ .

This is easier than the gradient method!!

eg  $V = 6V$  and  $I = 4A$

$$\Rightarrow E = V + Ir \Rightarrow 10 = 6 + 4r$$

$$\Rightarrow 4r = 10 - 6 \Rightarrow 4r = 4 \Rightarrow r = 1\Omega$$

iii)  $I_{sc}$  can be found when the external or load resistor  $R$  is short circuited ie  $R=0$ .

Two methods can be used to find  $I_{sc}$ .

METHOD 1 FROM GRAPH.

$$I_{sc} \Rightarrow R=0 \therefore V=0$$

This occurs when the line cuts the x-axis

$$\therefore \underline{I_{sc} = 10A}$$

XXX Use METHOD 1 IF IT IS POSSIBLE XXX

METHOD 2 FROM EQN

$$E = V + Ir$$

$$\Rightarrow E = IR + Ir$$

as  $R=0 \Rightarrow I = I_{sc}$

$$\Rightarrow E = I_{sc} r$$

$$\Rightarrow I_{sc} = \frac{E}{r} = \frac{10}{1}$$


$$\Rightarrow \underline{I_{sc} = 10A}$$



## Ex8 - The Beast ('A' standard)

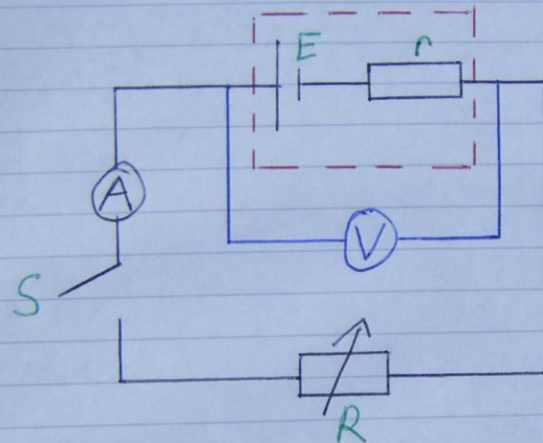(15)

To investigate the characteristics of a power supply unit, a student uses an ammeter and a variable resistor in the following circuit:



S open  
- V = Emf, E  
- A = 0A

S closed  
- V =  $V_{\text{load}}$ , V  
- A > 0A

Q a) From  $E = V + Ir$  show that  $R = \frac{E}{I} - r$

A a)  $E = V + Ir \Rightarrow E = IR + Ir$

$$\Rightarrow E - Ir = IR$$

then divide each side by I

$$\Rightarrow \frac{E - Ir}{I} = \frac{IR}{I}$$

$$\Rightarrow \frac{E}{I} - \frac{Ir}{I} = \frac{IR}{I} \Rightarrow \frac{E}{I} - r = R$$

$$\Rightarrow \boxed{R = \frac{E}{I} - r} \quad \therefore \text{QED.}$$




(16)

- Q b) A graph of  $R \propto \frac{1}{I}$  is plotted using the readings below from the table.

$R(\Omega)$	0.1	0.3	0.5	0.7	0.9	1.0
$\frac{1}{I}(A^{-1})$	0.35	0.55	0.75	0.95	1.15	1.25

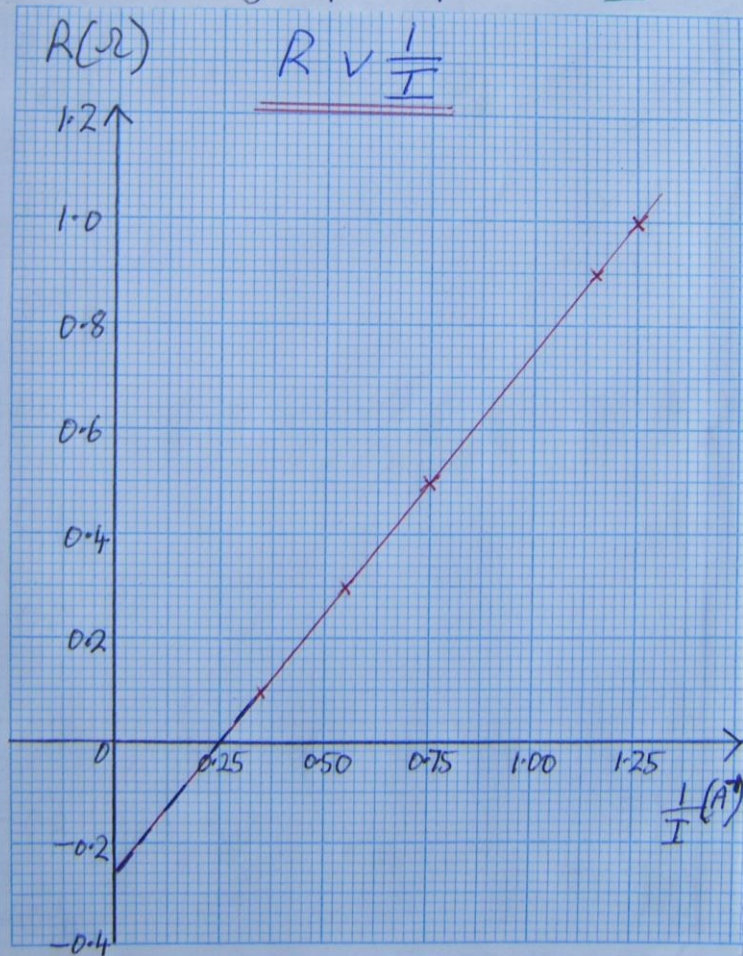- 1) Plot the graph of  $R \propto \frac{1}{I}$





Q // ii) Why is a graph of  $R \propto \frac{1}{I}$  drawn?

A // From  $E = V + Ir \Rightarrow R = \frac{E}{I} - r$

This equation with  $R$  as the subject of the formula can be compared with  $y = mx + c$ .

ie  $R = \frac{E}{I} - r$  with  $y = mx + c$

$\Rightarrow y = R$

$x = \frac{1}{I}$

$m = E \leftarrow$  gradient

$c = -r \leftarrow$  y-intercept

Q // iii) Find the gradient of the line which is the emf of the power supply unit.

A // iii)  $E =$  gradient  $m$

2 points from the line  $(0.55, 0.3)$  and  $(0.95, 0.7)$

$E = m = \frac{y_2 - y_1}{x_2 - x_1} = \frac{0.7 - 0.3}{0.95 - 0.55} = \frac{0.4}{0.4}$

$\therefore E = m = \underline{\underline{1V}}$

Q iv) Find  $r$ , the internal resistance of the power supply unit.

A iv)  $C = -r \Rightarrow C = -0.25$  from the graph.

$$\Rightarrow -0.25 = -r \Rightarrow \underline{\underline{r = 0.25 \Omega}}$$

Q v) Find  $I_{sc}$ , the short circuit current.

A v) In a short circuit,  $R=0$  and  $V=0$  (From  $V=IR$ ).

From the graph  $R=0$  when the line cuts the  $x$ -axis.


$$\frac{1}{I_{sc}} = 0.25 \Rightarrow I_{sc} = \frac{1}{0.25}$$

$$\Rightarrow \underline{\underline{I_{sc} = 4A}}$$



Ex9

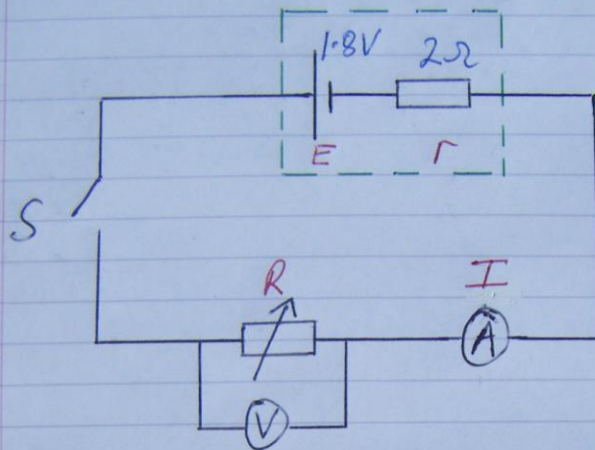The circuit below is used to investigate electrical power transfer in a circuit.



By varying the external resistor  $R$  and measuring the corresponding **current** and **potential difference** values, it is possible to determine the **power** delivered to the external circuit.

A set of results were taken from the experiment above and put into the table below.

$R(\Omega)$	7.0	4.0	2.5	1.6	1.0	0.6
$I(A)$	0.2	0.3	0.4	0.5	0.6	0.7
$V_R(V)$						
$P(W)$						

Q a) Complete the last two rows of the table.

b) Draw a graph of  $P(W)$  vs  $R(\Omega)$




c) i) From the graph identify the external resistance  $R$  when the maximum power  $P$  is transferred.

ii) How does this external resistance  $R$  compare with the internal resistance  $r$  in the circuit?

iii) What conclusion can be made from this experiment?

A a)

$R(\Omega)$	7.0	4.0	2.5	1.6	1.0	0.6
$I(A)$	0.2	0.3	0.4	0.5	0.6	0.7
$V_R(V)$	1.40	1.20	1.00	0.80	0.60	0.42
$P(W)$	0.28	0.36	0.40	0.40	0.36	0.29

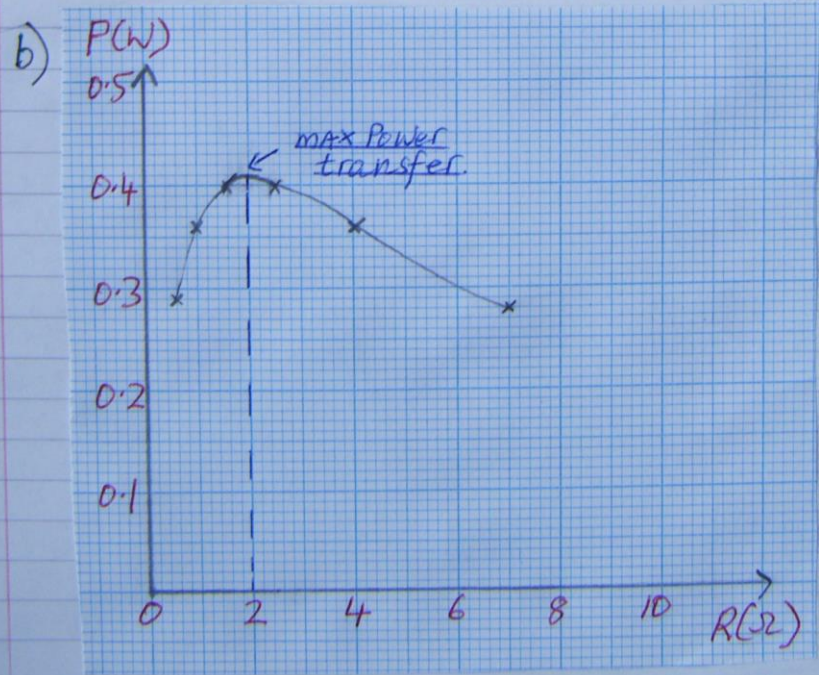



- c) i) From the graph produced the external resistance  $R = 2\Omega$  when the maximum power  $P$  is transferred.
- ii) At maximum power transfer  $r = R$  is  $2\Omega$ , the same.
- iii) The maximum power transferred in a circuit occurs when the internal resistance = external resistance.
- \* Remember that the term load resistance is often used instead of external resistance. \*