




# Wheatstone Bridge Circuits - B. McMullen <sup>①</sup>

What purpose do they have?  
These circuits can measure resistances that are unknown to a great degree of accuracy and precision.


NAT 5 → The methods used to examine/measure resistance have flaws that we will examine.

CIRCUIT A

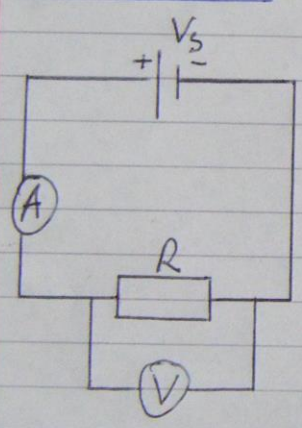

Precise and accurate for low resistances  
eg  $10\Omega$

CIRCUIT B

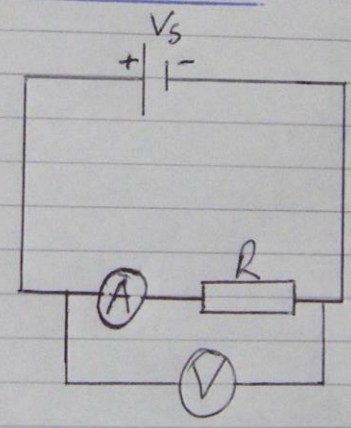

Precise and accurate for high resistances  
eg  $8000\Omega$


Neither of these set ups are suitable for MID-RANGE resistances eg  $400\Omega$  or  $80\Omega$ .

## EXTRA INFORMATION


- —  $\text{A}$  — ⇒ have a very low resistance
- —  $\text{V}$  — ⇒ have a very high resistance.

## Wheatstone Bridge Formations. (2)

### 1) Rectangular

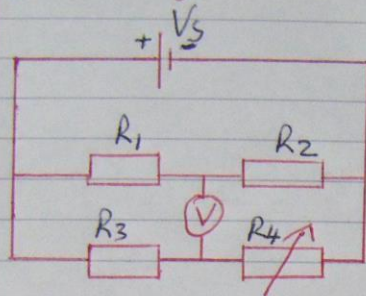

### 2) Diamond

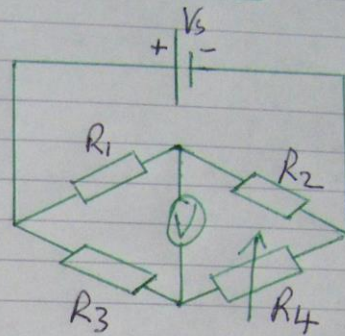

We can use an  $\text{---}\text{A}\text{---}$  or  $\text{---}\text{V}\text{---}$  or a galvanometer  $\text{---}\text{G}\text{---}$ .

\* (A galvanometer is simply a very sensitive  $\text{---}\text{A}\text{---}$  or  $\text{---}\text{V}\text{---}$ ) \*

- $R_4$  above is an unknown variable resistor.
- $R_4$  is varied until the reading on  $\text{---}\text{V}\text{---} = 0\text{V}$ . This is the balance point of the Wheatstone Bridge circuit.

Balance point equation

$$\boxed{\frac{R_1}{R_2} = \frac{R_3}{R_4}}$$


OR

$$\boxed{\frac{R_1}{R_3} = \frac{R_2}{R_4}}$$

Ex 1

(3)

Q

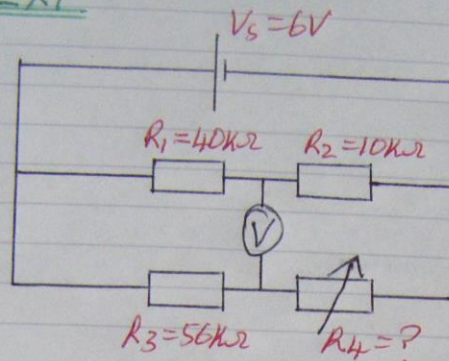

a) Calculate  $R_4$  when the bridge is balanced.

b) What is the reading on  $\text{V}$  when the bridge is balanced?

A a)  $\frac{R_1}{R_2} = \frac{R_3}{R_4}$

$$\Rightarrow \frac{40}{10} = \frac{56}{R_4}$$

$$\Rightarrow 40R_4 = 56 \times 10$$

$$\Rightarrow R_4 = \frac{56 \times 10}{40} = \underline{\underline{14k\Omega}}$$

b) When the bridge is balanced  $\text{V} = \underline{\underline{0V}}$ .

Q c) What affect would increasing the supply voltage to 10V have on the reading on the voltmeter if:

- i) Bridge is balanced
- ii) Bridge is unbalanced.

A c) i) When the bridge is balanced there would be no change i.e.  $\text{V} = 0V$

ii) When the bridge is unbalanced the reading on  $\text{V}$  would increase.


## Power Equations

(4)

Power is the energy transformed per second.

$$\text{Power} = \frac{\text{Energy}}{\text{Time}}$$

(Watts) (Joules) (seconds)

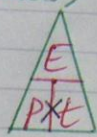

1/  $E = Pt$

2/  $P = \frac{E}{t}$


3/  $t = \frac{E}{P}$

## Three Electrical Power Equations

- $P = IV$   $\Rightarrow P = IV \Rightarrow I = P/V \Rightarrow V = P/I$
- $P = I^2R$   $\Rightarrow P = I^2R \Rightarrow I^2 = P/R \Rightarrow R = P/I^2$
- $P = V^2/R$   $\Rightarrow P = V^2/R \Rightarrow V^2 = PR \Rightarrow R = V^2/P$

## Ex 2

Q

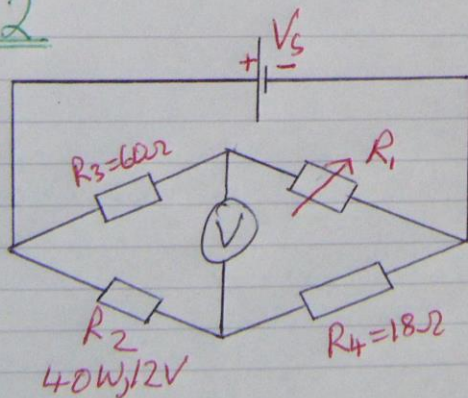

a) Calculate the resistance  $R_2$

b) Find  $R_1$  when the bridge is balanced.

5

A a)  $P = \frac{V^2}{R} \Rightarrow R = \frac{V^2}{P} = \frac{12^2}{40} = \frac{144}{40} = \underline{\underline{3.6\Omega}}$


b)  $\frac{R_3}{R_2} = \frac{R_1}{R_4}$

Top left over bottom left = Top right over bottom right

$\Rightarrow \frac{60}{3.6} = \frac{R_1}{18}$

$\Rightarrow R_1 = \frac{60 \times 18}{3.6} = \underline{\underline{300\Omega}}$

EX3

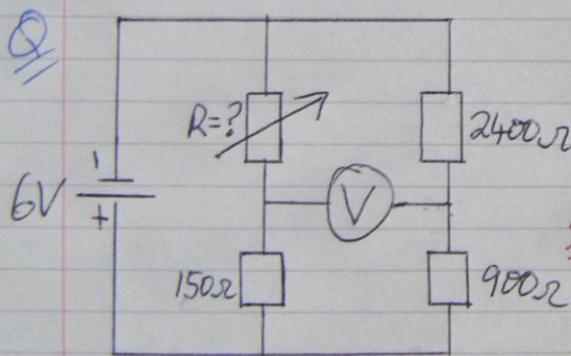

Calculate R when the bridge is balanced.

A  $\frac{R_1}{R_2} = \frac{R_3}{R_4}$

$\Rightarrow \frac{150}{900} = \frac{R}{2400}$


$\Rightarrow R = \frac{150 \times 2400}{900}$

$\Rightarrow \underline{\underline{R = 400\Omega}}$

\* Rotate the circuit so that the supply is on the top \*

## Unbalanced Wheatstone Bridges

(6)

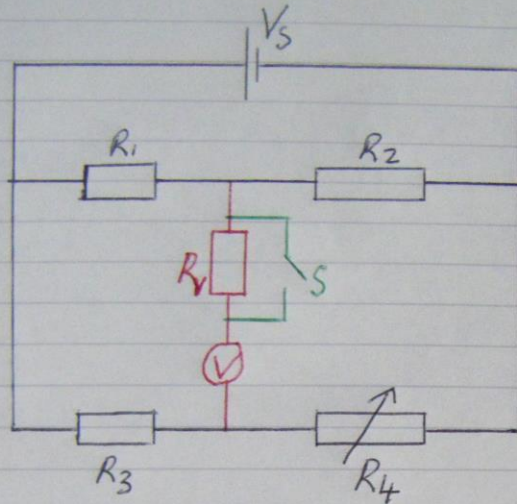


• When the bridge is balanced  $V = 0$


• When the bridge is highly out of balance  $V = \text{large}$

•  $R_v$  protects  $V$  when the bridge is highly out of balance.

- $R_4$  is varied until the reading on  $V$  decreases until it is near the balance point.
- The switch  $S$  is then closed which short circuits resistor  $R_v$ .
- The voltmeter then becomes more sensitive to very small variations in current or voltage.
- At balance point  $V = 0$ .

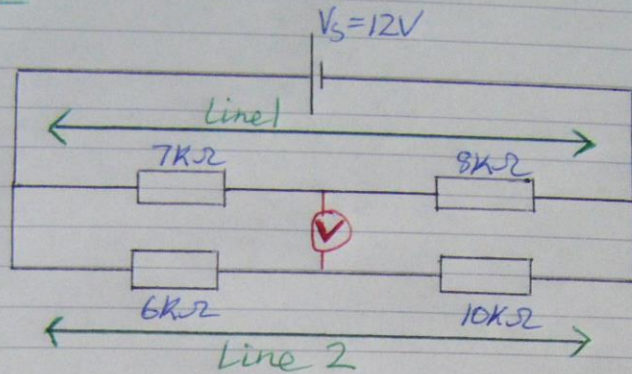Unbalanced Wheatstone Bridge calculation <sup>(7)</sup>  
Ex4



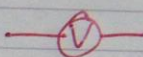Calculate the reading on 

Use the 'Beer Equation'

$$\text{XXX } V_2 = \left( \frac{R_2}{R_1 + R_2} \right) \times V_s \text{ XXX}$$

Line 1 7kΩ and 8kΩ

$$V_{7k} = \left( \frac{7}{8+7} \right) \times 12V = \frac{7}{15} \times 12V = \underline{\underline{5.6V}}$$

$$V_{8k} = \left( \frac{8}{7+8} \right) \times 12V = \frac{8}{15} \times 12V = \underline{\underline{6.4V}} \quad \checkmark$$

$$\text{Check } V_s = V_{7k} + V_{8k} \Rightarrow 12V = 5.6V + 6.4V$$

Line 2 6kΩ and 10kΩ

$$V_{6k} = \left( \frac{6}{10+6} \right) \times 12V = \frac{6}{16} \times 12V = \underline{\underline{4.5V}}$$

⑧

$$V_{10K} = \left( \frac{10}{6+10} \right) \times 12V = \frac{10}{16} \times 12V = \underline{\underline{7.5V}}$$

check  $V_s = V_{6K} + V_{10K} = 4.5V + 7.5V = 12V$  ✓

$$\text{---} \text{Ⓧ} \text{---} = 5.6V - 4.5V = \underline{\underline{1.1V}}$$


(LMS)

OR

$$\text{---} \text{Ⓧ} \text{---} = 7.5V - 6.4V = \underline{\underline{1.1V}}$$

(RHS)


### Wheatstone Bridge Experiment

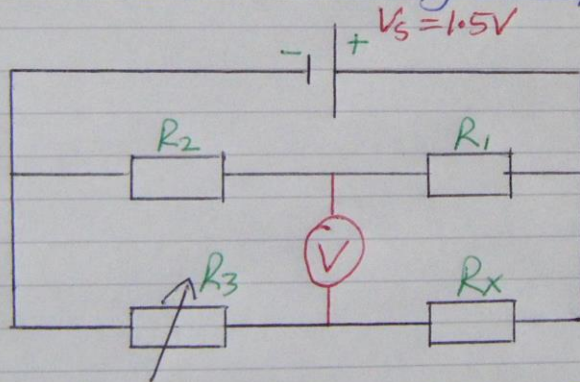

Reading on Ⓧ (V)	$R_3(\Omega)$	$\Delta R_3(\Omega)$
• -0.8	1960	-200
• -0.4	2060	-100
• 0	2160	0
• +0.4	2260	+100
• +0.8	2360	+200

→ Bridge is balanced here!!



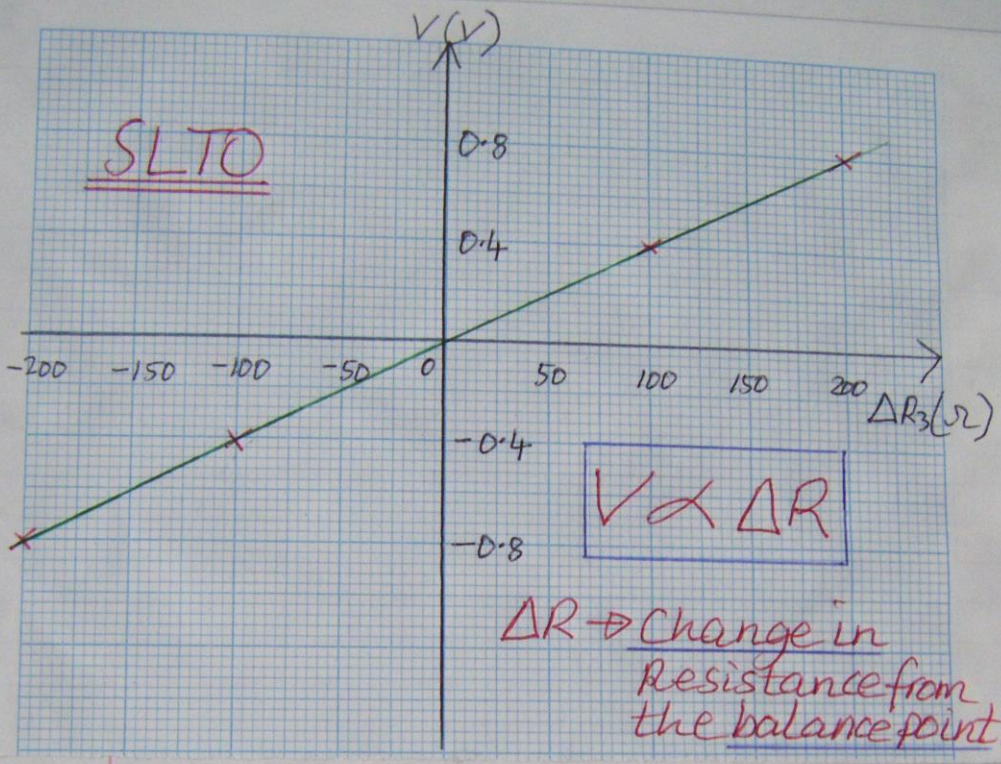

Conclusion


The out of balance current or voltage is directly proportional to the change in resistance ( $\Delta R$ ) away from the balance point.

## metre Bridge

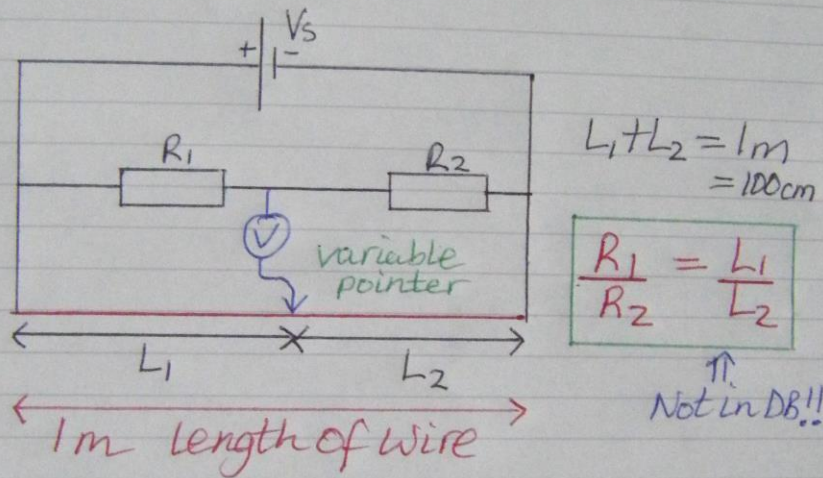(10)

This is a variation of the standard Wheatstone Bridge Circuit.

It contains two resistors and a metre length of wire rather than the standard four resistors.



### Ex5

Q From the metre bridge circuit above, find  $L_1$  and  $L_2$  from the combination of resistances below:

a)  $R_1 = 28\text{k}\Omega$  and  $R_2 = 12\text{k}\Omega$

b)  $R_1 = 8\text{k}\Omega$  and  $R_2 = 32\text{k}\Omega$

(11)

• A a)  $\frac{R_1}{R_2} = \frac{L_1}{L_2} \Rightarrow \frac{28}{12} = \frac{L_1}{L_2}$

$$\Rightarrow \frac{7}{3} = \frac{L_1}{L_2}$$

$$\Rightarrow \underline{L_1 = 70\text{cm}} \text{ and } \underline{L_2 = 30\text{cm}}$$

b)  $\frac{R_1}{R_2} = \frac{L_1}{L_2} \Rightarrow \frac{8}{32} = \frac{L_1}{L_2}$

$$\Rightarrow \frac{1}{4} = \frac{L_1}{L_2}$$

$$\Rightarrow \underline{L_1 = 20\text{cm}} \text{ and } \underline{L_2 = 80\text{cm}}$$