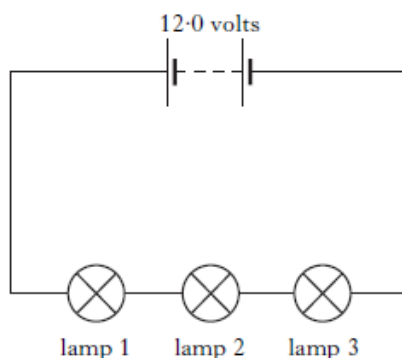


# Electricity 1 Questions – NAT 5

1) Three identical lamps are connected as shown in **circuit 1**.


A 12.0V battery supplies a current of 0.2 A.



*Circuit 1*

- a) i) State the current in lamp 1.  
 ii) Calculate the voltage across lamp 1.
- b) The lamps are now connected as shown in **circuit 2**.

The 12.0V battery supplies a current of 0.4A.

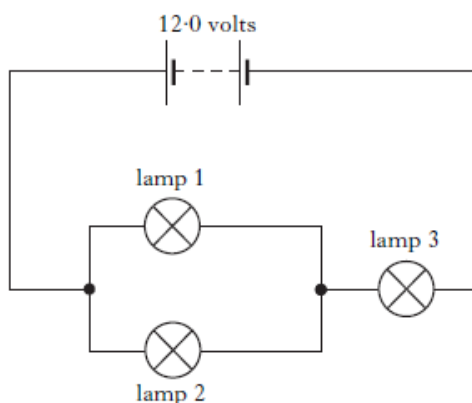

*Circuit 2*

- i) Complete the table to show the **current passing through** each lamp and the **voltage dropped across** each lamp.


	<i>Lamp 1</i>	<i>Lamp 2</i>	<i>Lamp 3</i>
<i>Voltage (volts)</i>			8.0
<i>Current (amperes)</i>			0.4

- ii) Calculate the power dissipated in lamp 3.  
 iii) State the **useful** energy change in a lamp.

2) A student sets up an experiment to investigate the current through and the voltage across two different resistors.

The student uses a battery, an ammeter, a voltmeter and some wires to obtain measurements for each resistor.

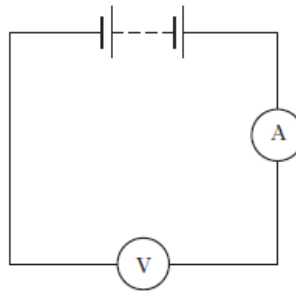a) Complete the diagram below by inserting a resistor, to show how the measurements could be obtained.




b) The measurements obtained for each resistor are shown in the table below.

<i>Resistor</i>	<i>Current (amperes)</i>	<i>Voltage (volts)</i>
X	0.6	1.5
Y	7.5	1.5

- i) Use the information to calculate the resistance of resistors X and Y.
- ii) When the resistance of the circuit increases, what happens to the current flowing in the circuit?

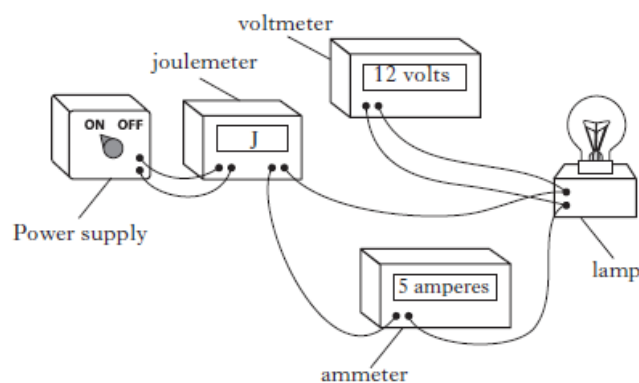3) A student sets up the following experiment to investigate the power of a filament lamp.




The reading on the voltmeter is 12V and the reading on the ammeter is 5A.

Calculate or find:

- a) Resistance of the lamp.
- b) Power dissipated in the lamp.

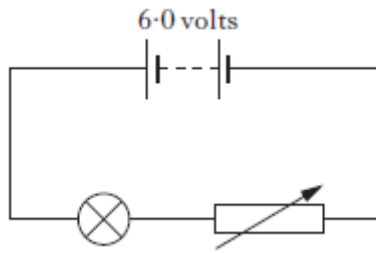4) A student is investigating the operation of a filament lamp using the following circuit.




When the **voltage across** the lamp is 2V the **current through** the lamp is 0.2A.

- a) Calculate the power dissipated in the lamp.
- b)
  - i) Calculate the resistance of the lamp.
  - ii) Calculate the voltage across the variable resistor.
- c) The resistance of the variable resistor is increased.
  - i) What happens to the brightness of the lamp?
  - ii) Explain your answer.

5) A car headlamp is rated at 60W. The light produced is 20% of the total energy transferred to the lamp.

Calculate the energy transferred as **light** in 10s.


6) A circuit is set up as shown below.

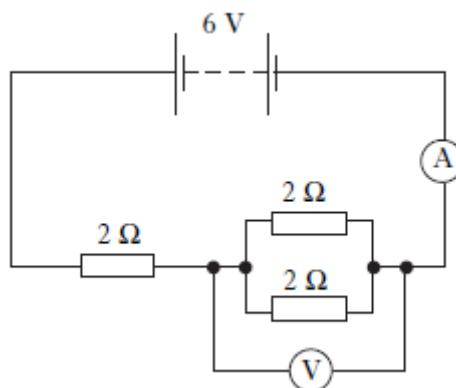

Calculate or find:

- a) Reading on the ammeter
- b) Reading on the voltmeter
- c) Power dissipated in the 2Ω resistor in series.


7) A circuit is set up as shown below.

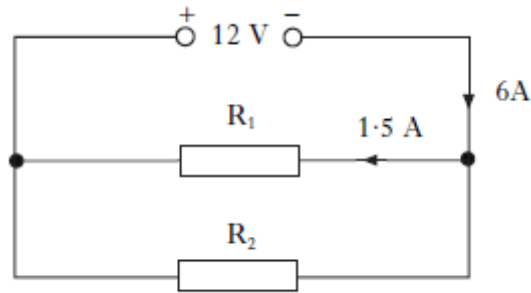

Calculate or find:


- Current through  $R_2$ .
- Potential difference across  $R_2$ .
- Resistance  $R_1$ .
  - Resistance  $R_2$ .

8) A circuit is set up as shown below.

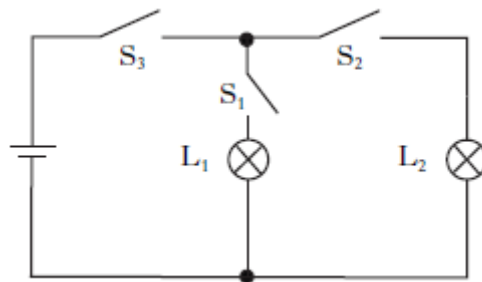

- Which switches must be closed to light up lamp  $L_1$ ?
- Which switches must be closed to light up lamp  $L_2$ ?

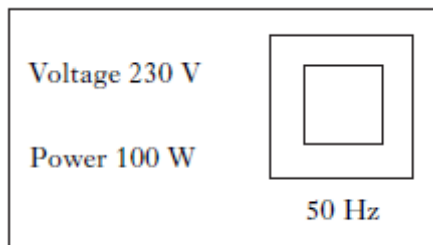9) The information show is for an electric food mixer.



Calculate or find:


- The current passing through the food mixer when it is operating.
- The resistance of the food mixer.

**10)** A charge of 15C passes through a resistor in 12s. The potential difference across the resistor is 6V.

Calculate or find:

- The current passing through the resistor.
- Power developed by the resistor.

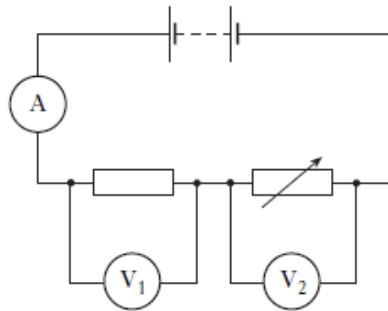**11)** A circuit is set up as shown below.




The resistance of the variable resistor is gradually reduced.

What will happen to:


- The reading on the ammeter?
- The reading on voltmeter  $V_1$ ?
- The reading on voltmeter  $V_2$ ?

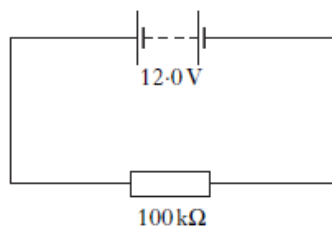**12)** A circuit is set up as shown below.



Calculate the power supplied to the resistor.

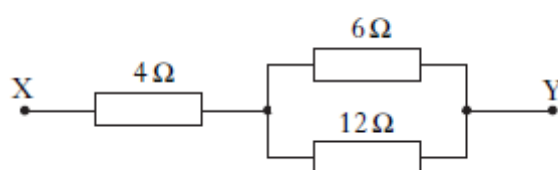**13)** Three resistors are connected as shown.




Calculate the total resistance between X and Y.


14) The mains voltage in the UK is 230V ac.

- What is the frequency of the mains supply in the UK?
- How does the peak voltage of the mains supply in the UK compare with 230V?

15) Identify the circuit symbols below.

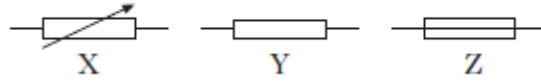

16) A circuit is set up as shown below.

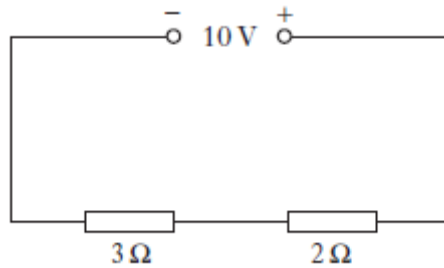


Calculate or find:

- The potential difference across the  $3\Omega$  resistor.
- The power developed across the  $3\Omega$  resistor.

17) Which of the following statements are true or false:

- In an ac circuit the direction of the current changes regularly.
- In a dc circuit the current flows in one direction only.
- In an ac circuit the size of the current stays constant.

18) A circuit is set up as shown below.

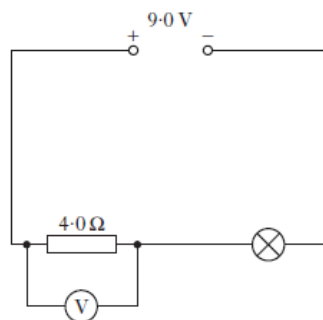

The current flowing through the lamp is 1.5A.

Calculate or find:

- The reading on the voltmeter.
- The power developed in the lamp.


19) A mobile phone contains a battery which is charged using a base unit. The base unit contains a transformer and is connected to the ac mains supply.



- What is the purpose of the mains supply?
- Name the supply mentioned that is dc.
- ac is short for alternating current.

Explain what is meant by alternating current.

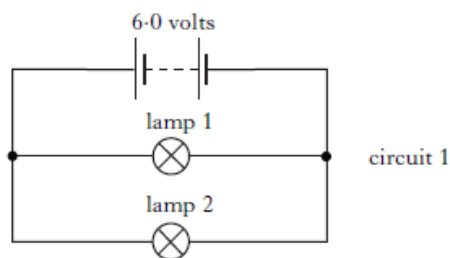20) Two identical lamps are connected to a 6.0V battery as shown in circuit 1.




- The battery supplies a current of 0.4A to the circuit.

Complete the table below to show the current in each lamp and the voltage across each lamp.

	Lamp 1	Lamp 2
Current (amperes)		
Voltage (volts)		

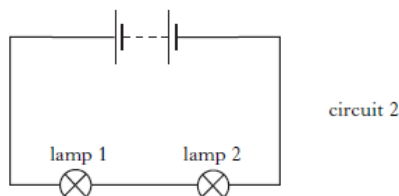
- The two lamps are now connected as shown in circuit 2.



State the voltage of the battery required to light the lamps with the same brightness as in circuit 1.


- In which of the two circuits, circuit 1 or circuit 2, would lamp 2 still be on when lamp 1 is removed?

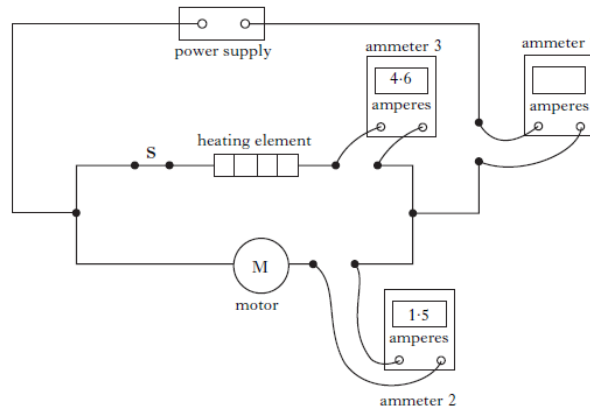**21)** A design uses three ammeters to measure the current, in amperes, at various points in the circuit of a model-sized electric fan heater.



- Calculate the reading on ammeter 1.
- What happens to the reading on ammeter 1 when the switch is opened?
- The full size mains heater has a rating plate for the UK supply stating its operational voltage and current.
  - Is the UK mains supply ac or dc?
  - State the value of the mains voltage in the UK.
  - State the value of the mains frequency in the UK.

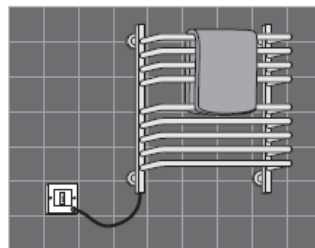**22)** A bathroom is fitted with an electrically heated towel rail. The towel rail is filled with water which is heated by a 300W electric heating element connected to the mains supply.



- State the declared value of the mains voltage.
- Calculate the current supplied to the towel rail when it is operational.
- Calculate the resistance of the towel rail.


**23)** The charge passing through an  $8\Omega$  resistor in 20 s is 80C.

Calculate or find:

- The current flowing through the resistor.
- The power developed in the resistor.
- The heat energy given off by the resistor over the 20s.



24) A circuit is set up as shown below.

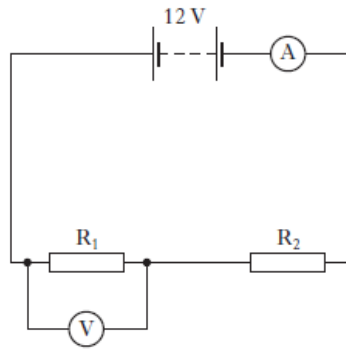

The reading on the ammeter is 3.0A and the reading on the voltmeter is 4.0V

Calculate or find:

- Resistance  $R_1$ .
- Resistance  $R_2$ .

25) A halogen heater contains four heater tubes which can be switched on separately or all together. The heater is mains operated.



- When one heating tube is switched on the current is 1.25A and the voltage across the tube is 230V.

Calculate the resistance of the tube.

- During cold weather the heater is used to heat a large conservatory.



The heater is switched on at its highest setting.

At this setting the heater has a power rating of 1600W.

The heater is operated for 8 hours each day for one week.

- Calculate the energy in kilowatt-hours used in this week.
- How much would it cost to run this heater for a week if it costs 15p per unit?